

Assembling Version 2 of the FM Converter Circuit Board

May 2026
Gord Rabjohn
VE3ILZ

Which version do you have?

- This document applies to version 2 of the board.
- If you have version 1 of the board, please refer to the OTHER FM_Converter_PCB_Assembly document.



Differences between V1 and V2: Physical (things that don't show up on the schematic)

- Enlarge the solder holes for the external connections.
- Place a hole behind the two potentiometers so they can be adjusted from either side of the board.
- Change layout around PLL to reduce noise coupled into the PLL input terminal.
- Some component had to be moved around.
- Added some labels.
- Note that the board size, mounting holes, general layout has not changed.


Differences between V1 and V2: Electrical (they show up on the schematic)

- Add provisions (R3, R6) for temperature compensation of the 4046 PLL.
- Add a few test points.
- Make a place for a resistor from VCO pin 9 to ground (see discussion of PLL stability).
- The negative voltage supply is now a doubler to make it more effective as an artificial AGC voltage.
- To make room, some components that were never used in the first version were removed (Resistor from U1 pin 2, C17, former R3).
- Add Q60 and R60 which can be used by the adventurous to make a converter that turns an AM/SW radio into an AM/FM radio (there is a separate document that describes this).


Component Differences between V1 and V2

Component	Version 1	Version 2	Why
R2	Not present	PLL pin 9 to ground	Added for improved stability
R3	Present, DNI	Temp Comp	For temp compensation of 4046
R6	Solder Jumper	Temp Comp	For temp compensation of 4046
SJ6	Not Present	Solder Jumper	Renamed from R6
C48	Not Present	Cap in doubler	Increases voltage from -ve supply
D44	Not Present	Diode in doubler	Increases voltage from -ve supply
C17	Present, DNI	Not Present	Removed to make room
Q60, R60	Not Present	Present	For experimenters


Version 2

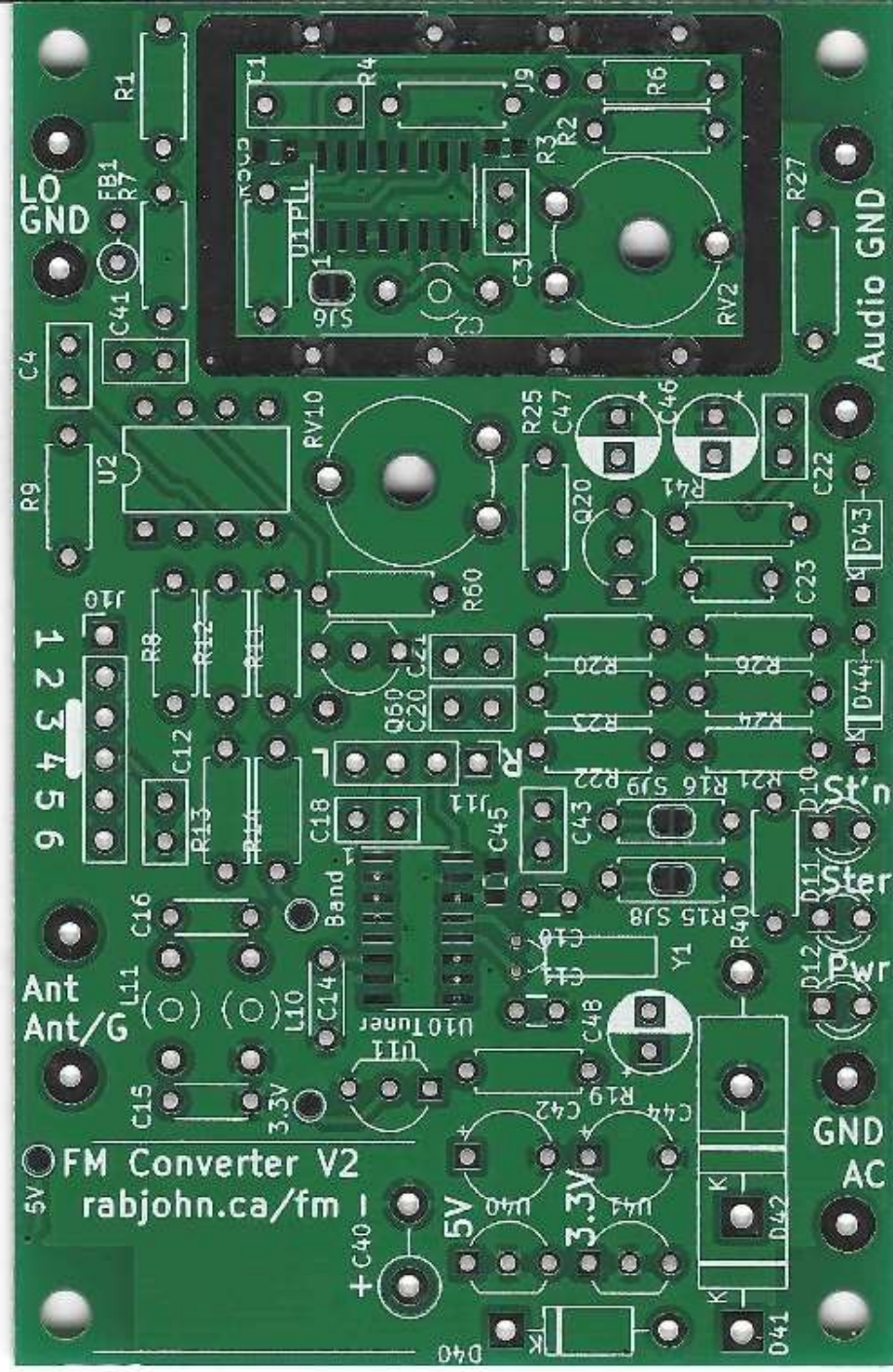


Version 1

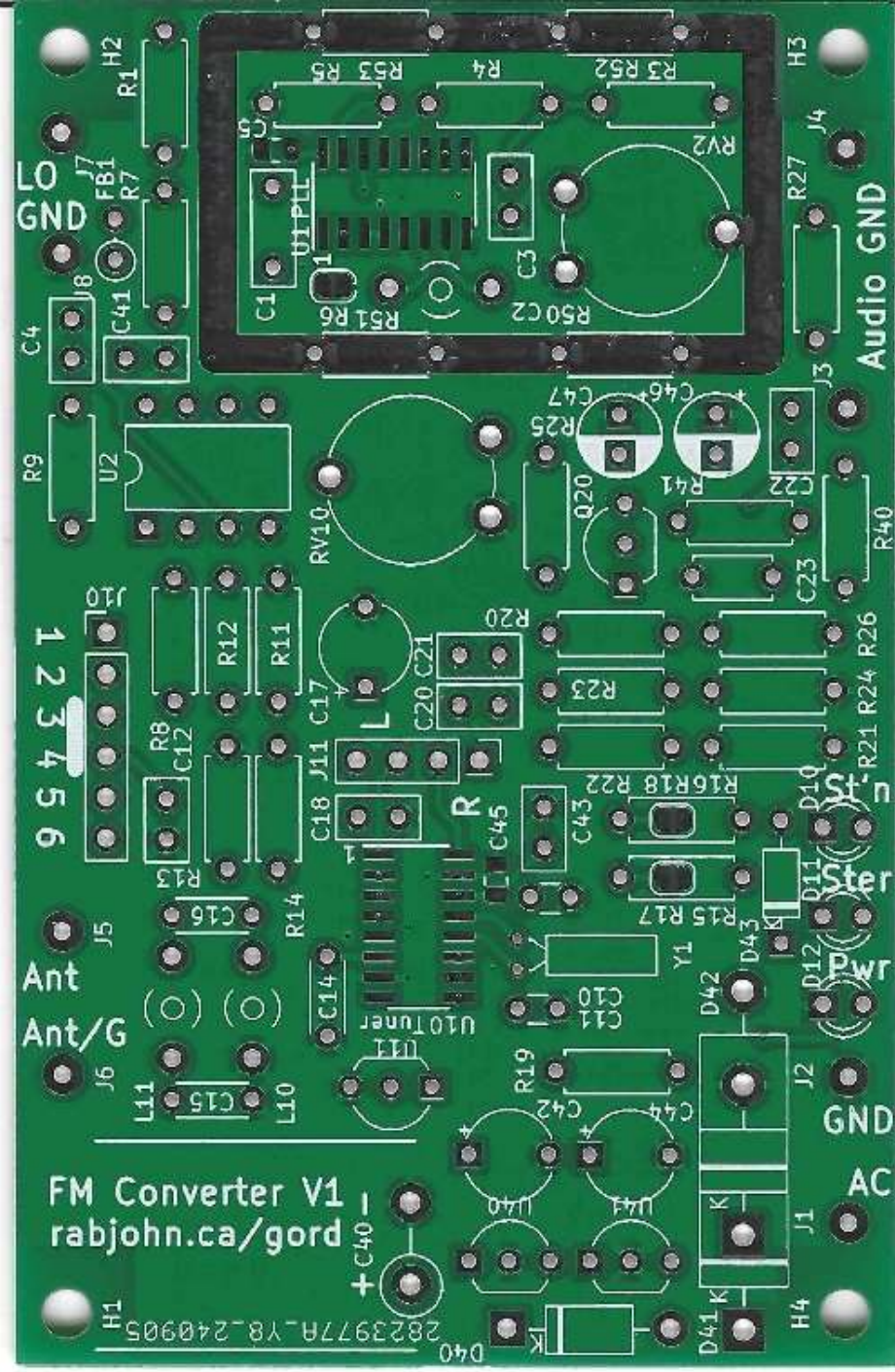


Version 2

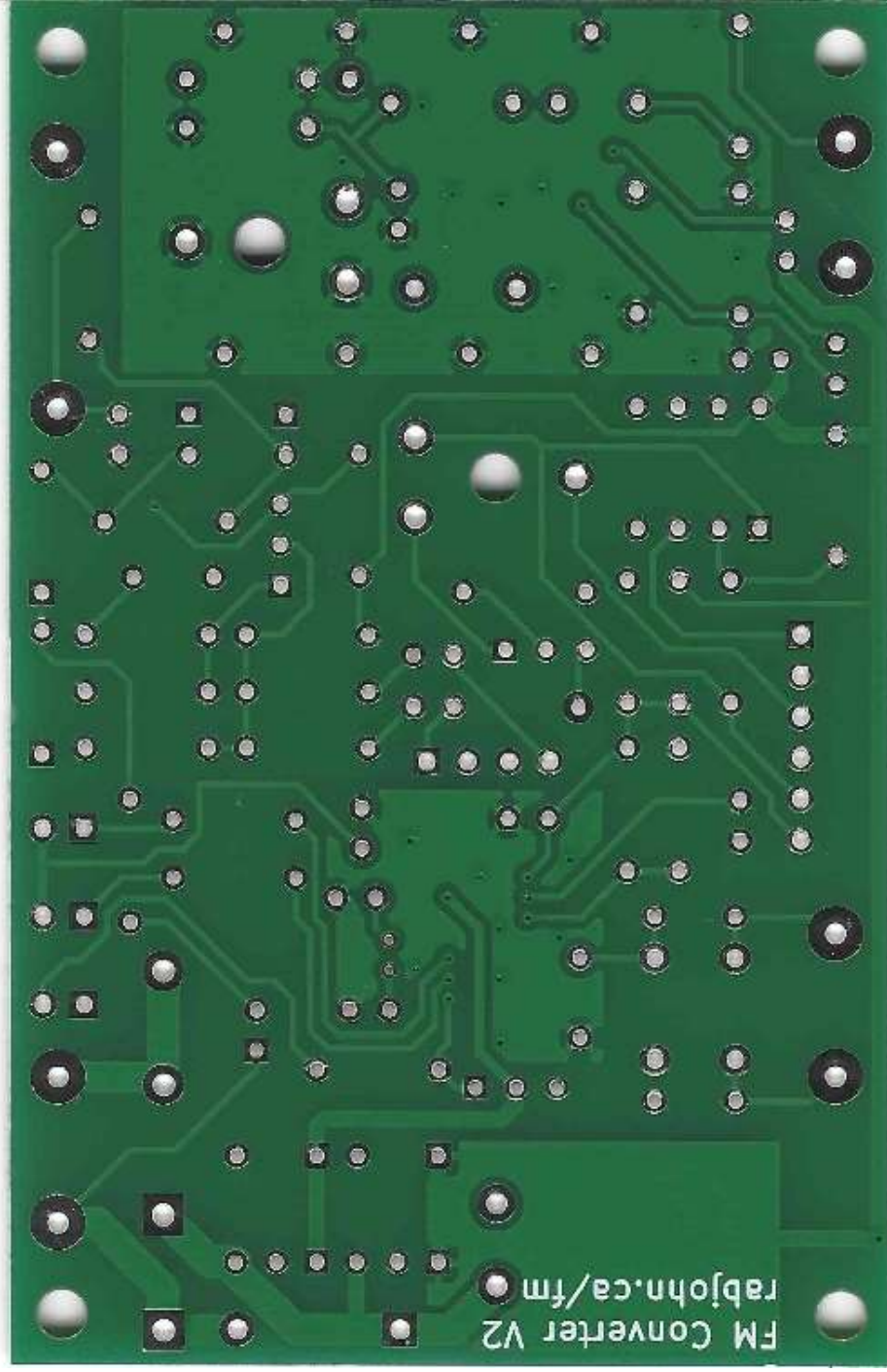

Version 1

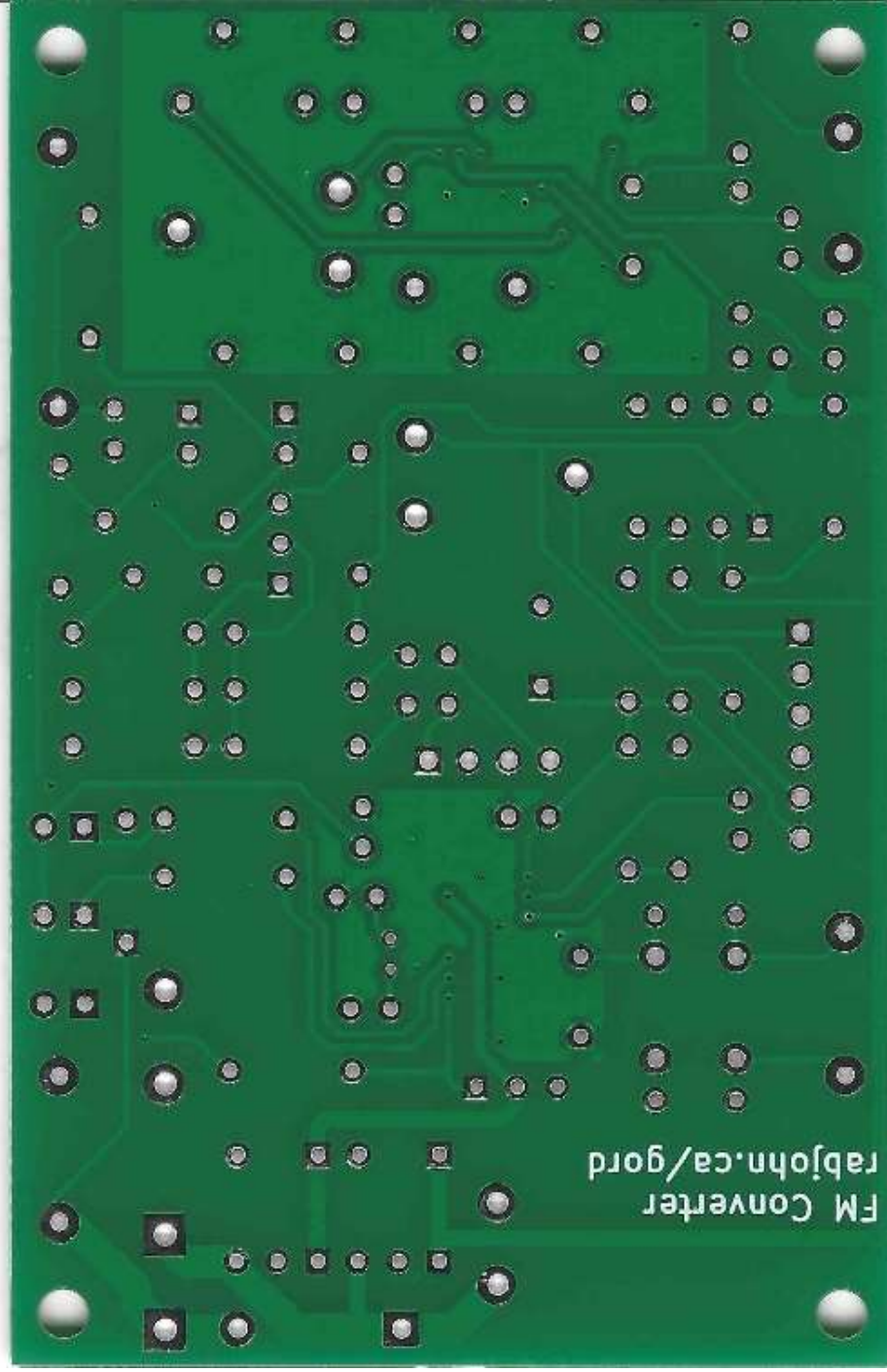

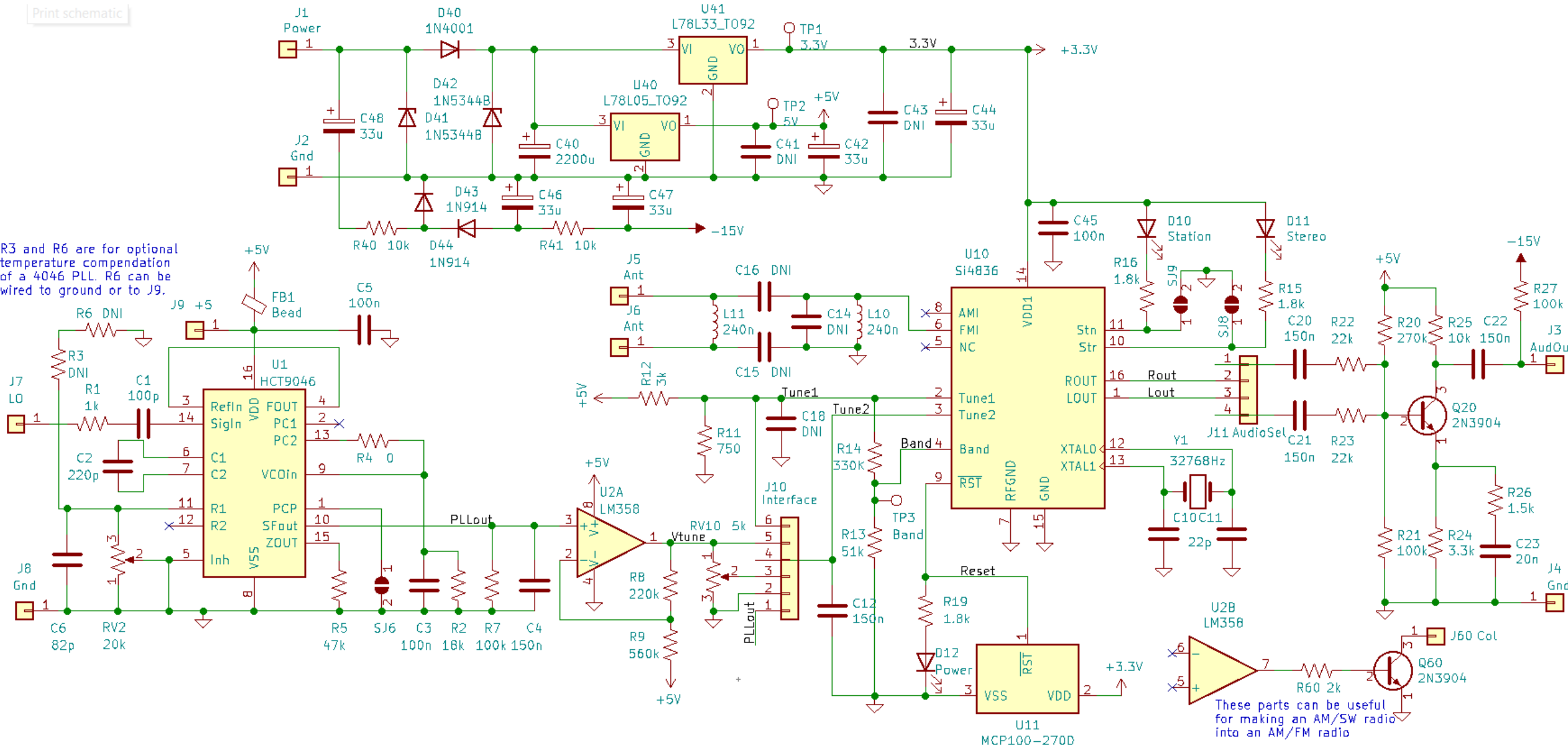

R3 and R6 are for optional temperature compensation of a 4046 PLL. R6 can be wired to ground or to J9.

These parts can be useful for making an AM/SW radio into an AM/FM radio

Power Supply

Level Shifter


Tuner

PLL

Audio Amp & -ve supply

Protection


LEDs

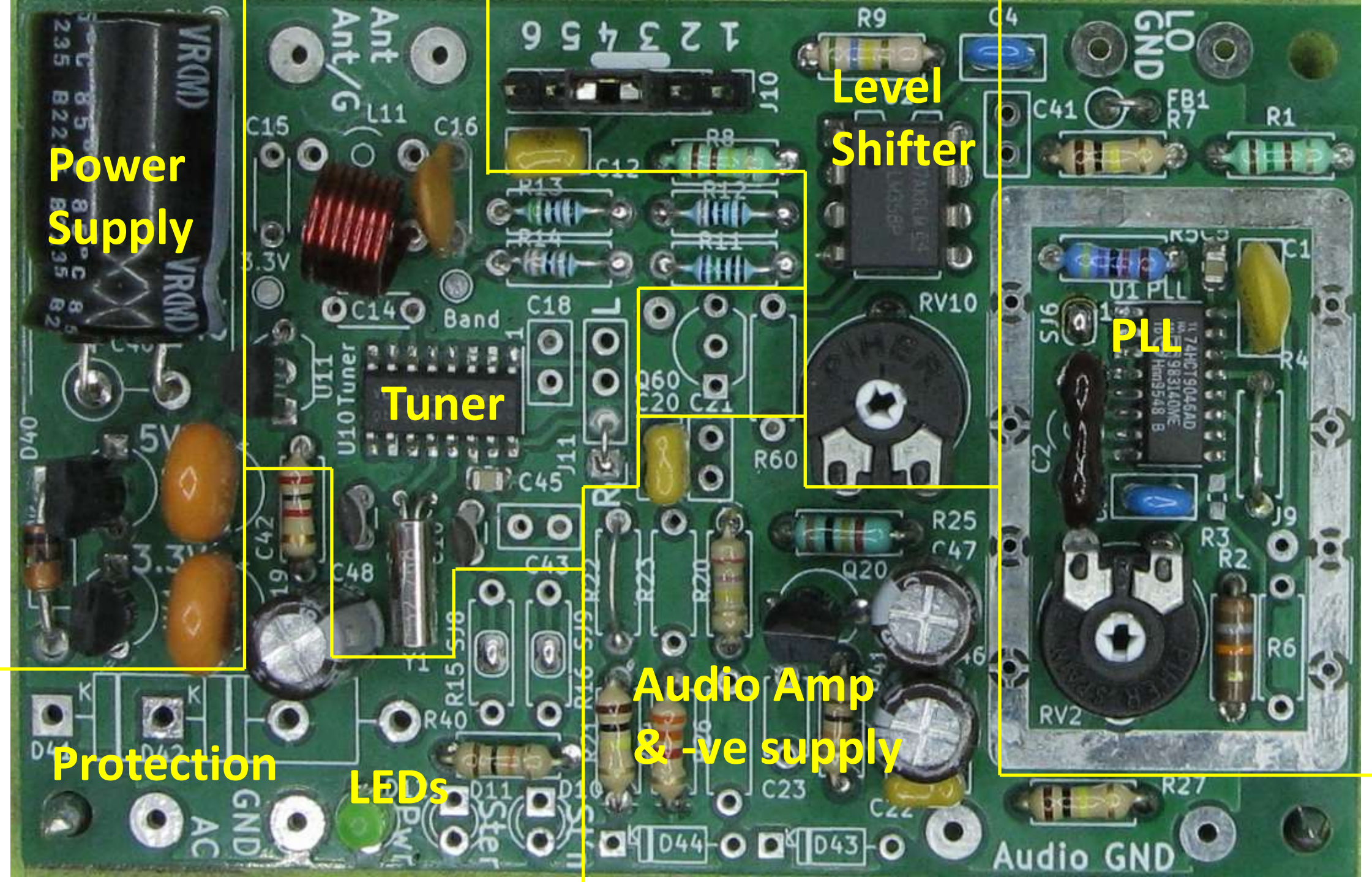

Choices

- Tuner chip: Use a Si4825 or a Si4836. Si4836 is stereo, and has indicator LEDs, but Si4825 is cheaper and works as well.
- Antenna coupling: Transformer coupling for a balanced twinlead antenna (like a folded dipole) or single-ended coupling for a single wire antenna. Single-ended is easy and works well.
- PLL chip: A 74HCT9046 is highly recommended. A 74HC4046 will do in a pinch but needs temperature compensation (discussed in main document).
- Higher voltage electrolytic caps needed if operated from 12VAC.
- Schottky rectifier and 5V LDO required if operated from 6VDC.
- Protection, negative DC supply: depends on application.

Assembly Instructions. 0. Bare Board

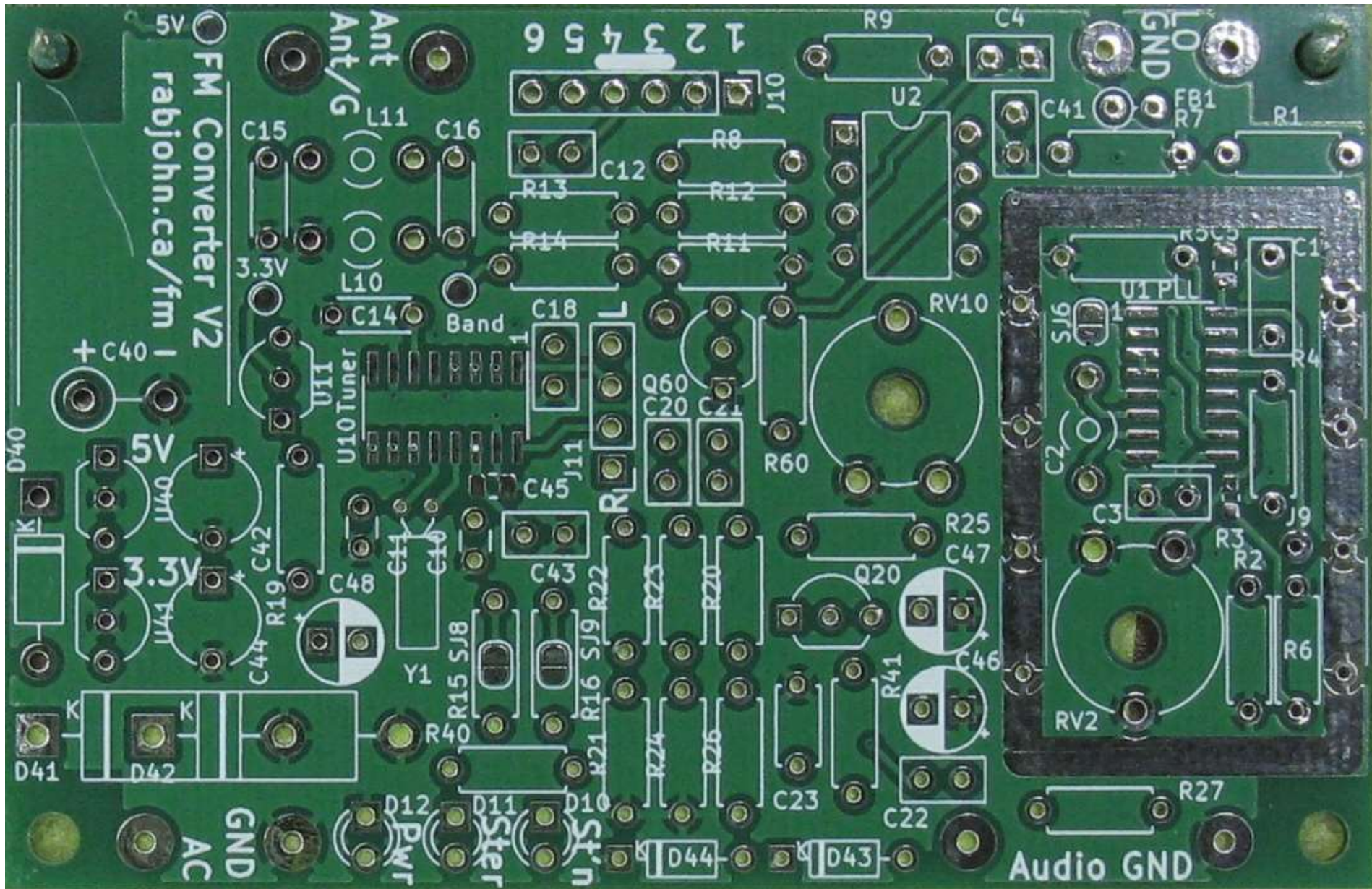


Soldering the SMT components

- I recommend using lead-tin solder paste. (lead-free is more difficult to work with) (this is not flux! this is solder in a paste form)
- Place paste on the solder pads for the two SMT ICs and the two SMT caps. You'll need a microscope unless you are very experienced. I use a toothpick.
- Plunk the ICs into the paste.
- I recommend: Use a hot plate to get the board up to ~100-150C, then use a fine tipped soldering iron for local heating. You can melt the solder paste on a single pin to secure the IC in place, then solder the rest of the pins one at a time. Easy to touch-up.
- Alternatively, reflow the solder paste using either:
 - Hot plate at about 220C
 - Hot air gun (use low air flow so you do not dislodge the components)
 - Oven (makes adjusting on-the-fly more difficult). Toaster oven may be OK.
- There are those who can do this all with just a fine soldering iron. Not me!
- Clean with flux remover. Remove excess solder paste.


Electrostatic Discharge Precautions

- Semiconductors (especially the integrated circuits) can be damaged by electrostatic discharge (ESD).
- Familiarize yourself with proper handling procedures.
- Days with low humidity are the worst. Cold winter days are particularly bad, and can be exacerbated because of thick sweaters that generate static electricity. Use an ESD smock.
- Use a wrist strap to leak charge off of your body.
- Make sure the soldering iron tip has a path to ground.
- Keep parts in their ESD-safe bags until they are needed.

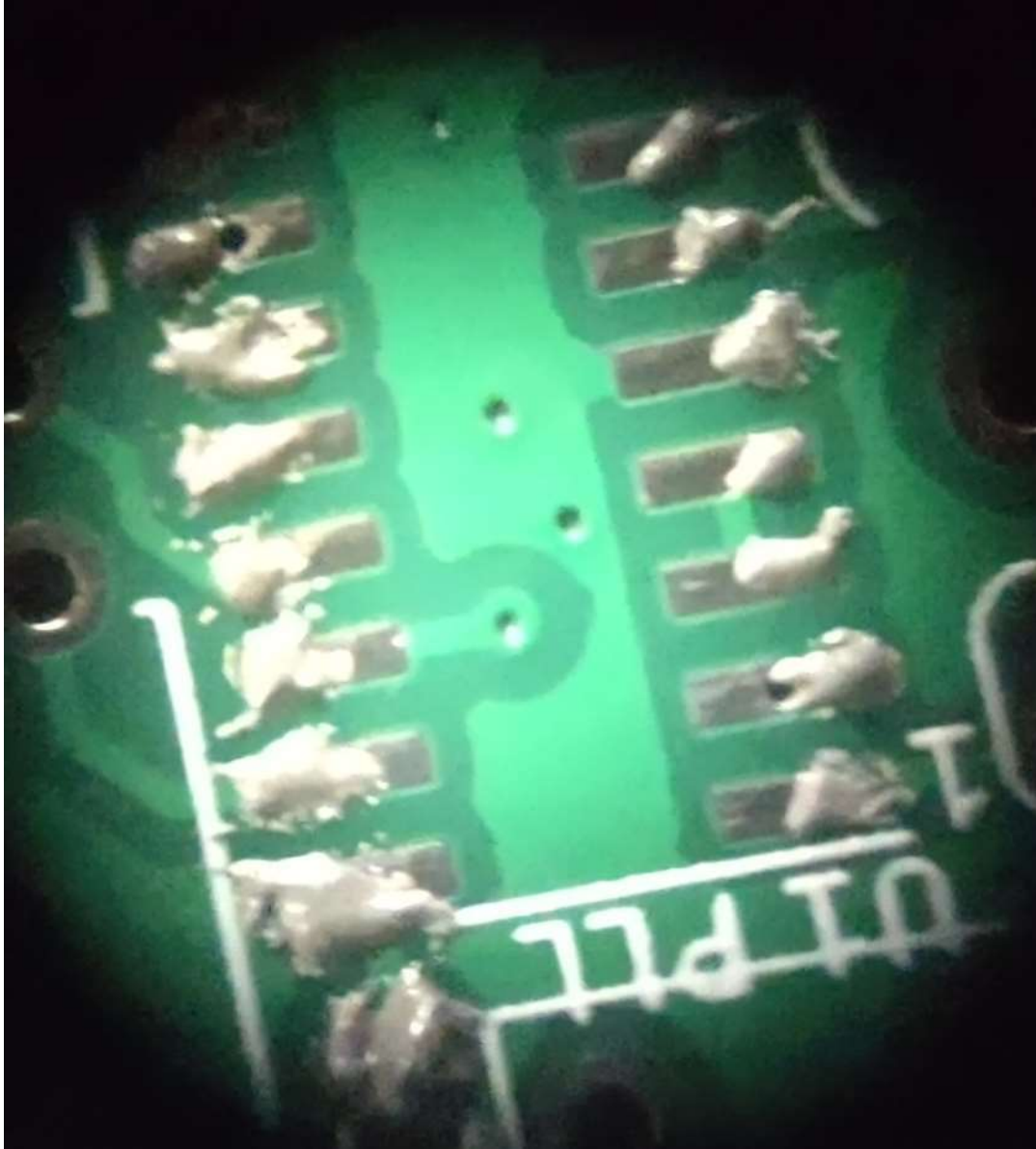Assembly Instructions. 1. SMD
Blobs of solder paste on each pad



Drop the IC into the paste

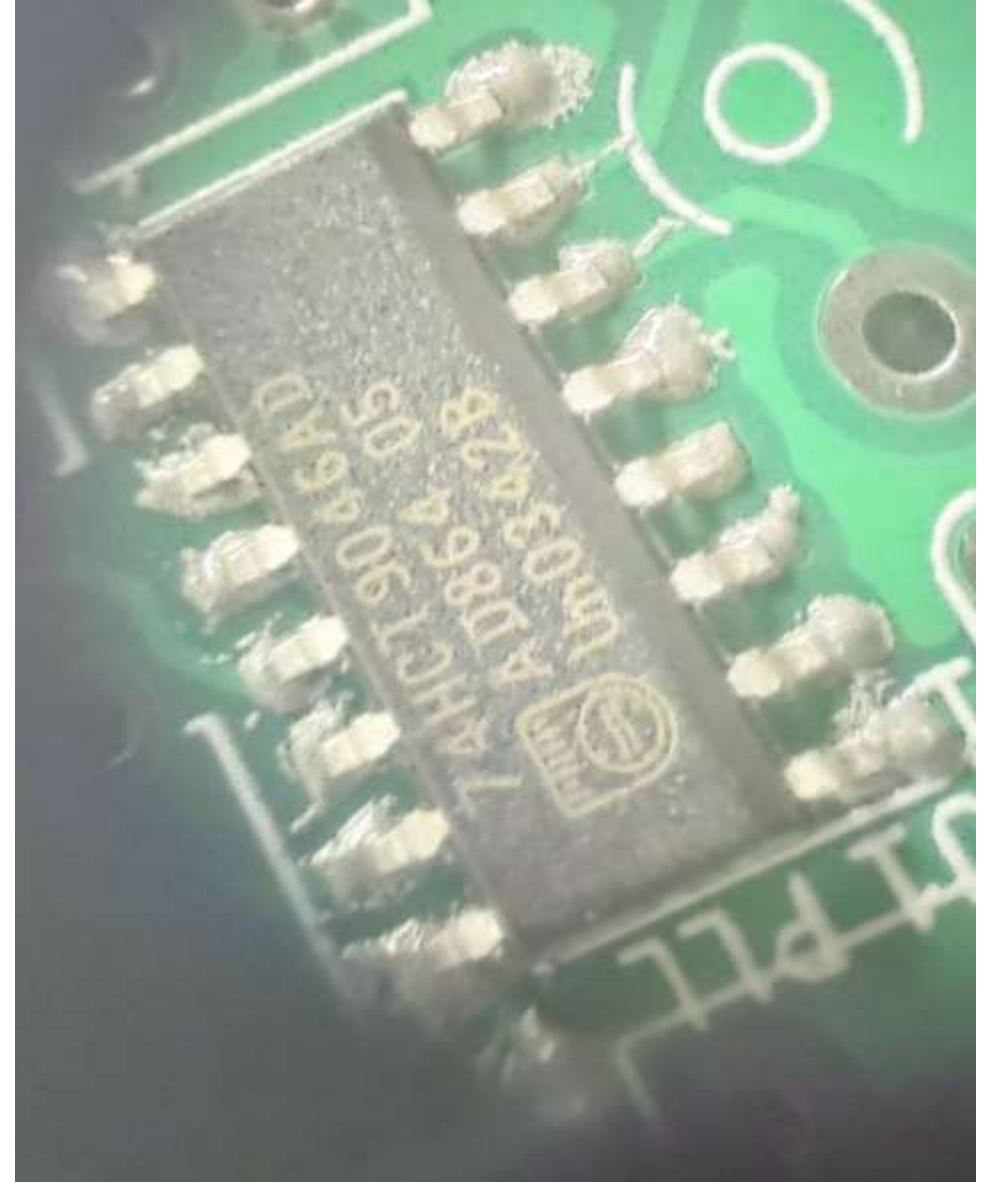


Assembly Instructions. 1. SMD

Heat the board to ~100-150 C.

Reflow one pin with a fine-tip iron to get the IC in the right location.

Reflow each pin..

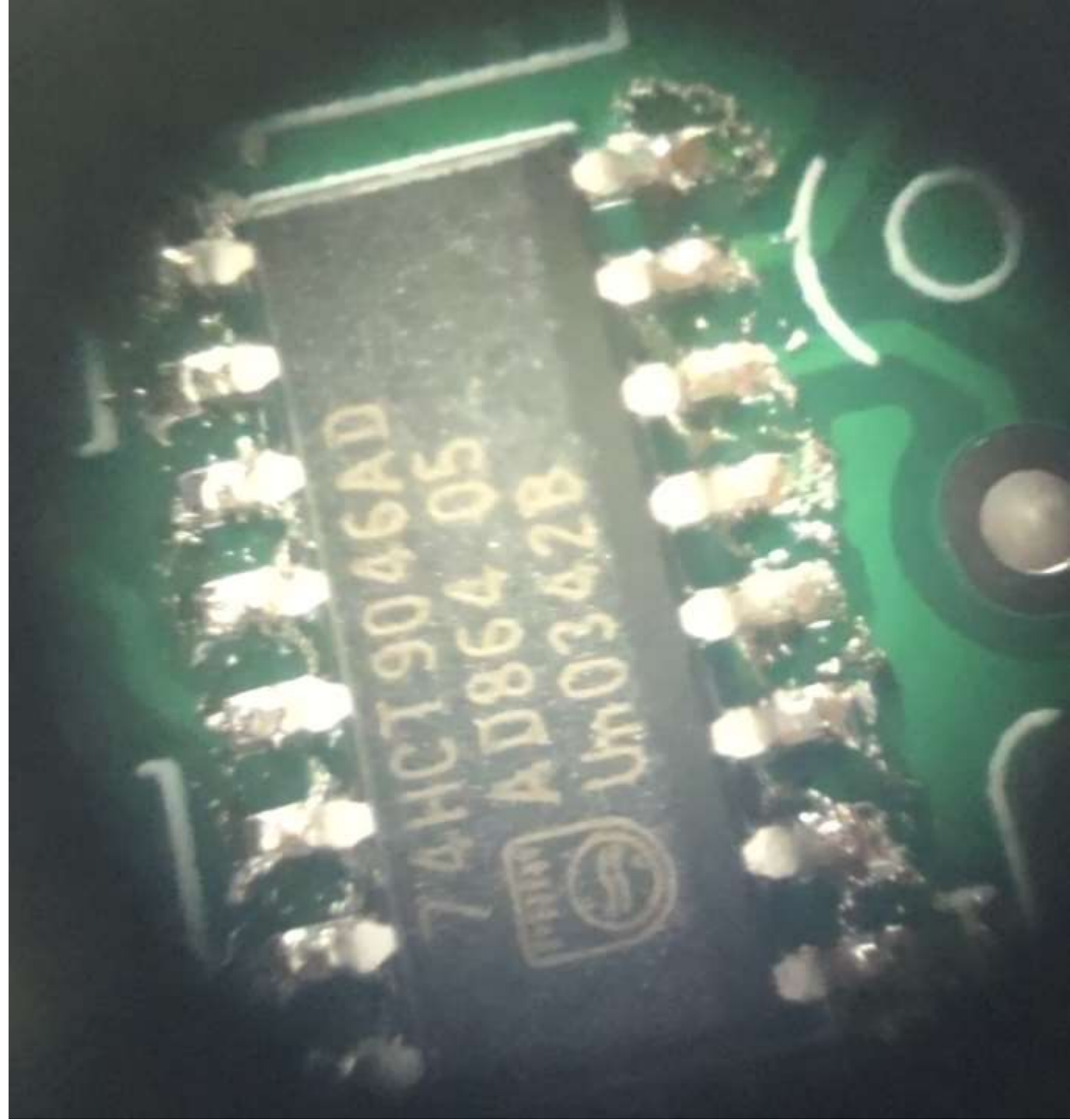Solder-wick can remove excess solder if necessary.



Assembly Instructions. 1. SMD
Clean the board up with flux remover. Inspect each pin.


Before Flux Cleaning




After Flux Cleaning



Assembly Instructions. 1. SMD

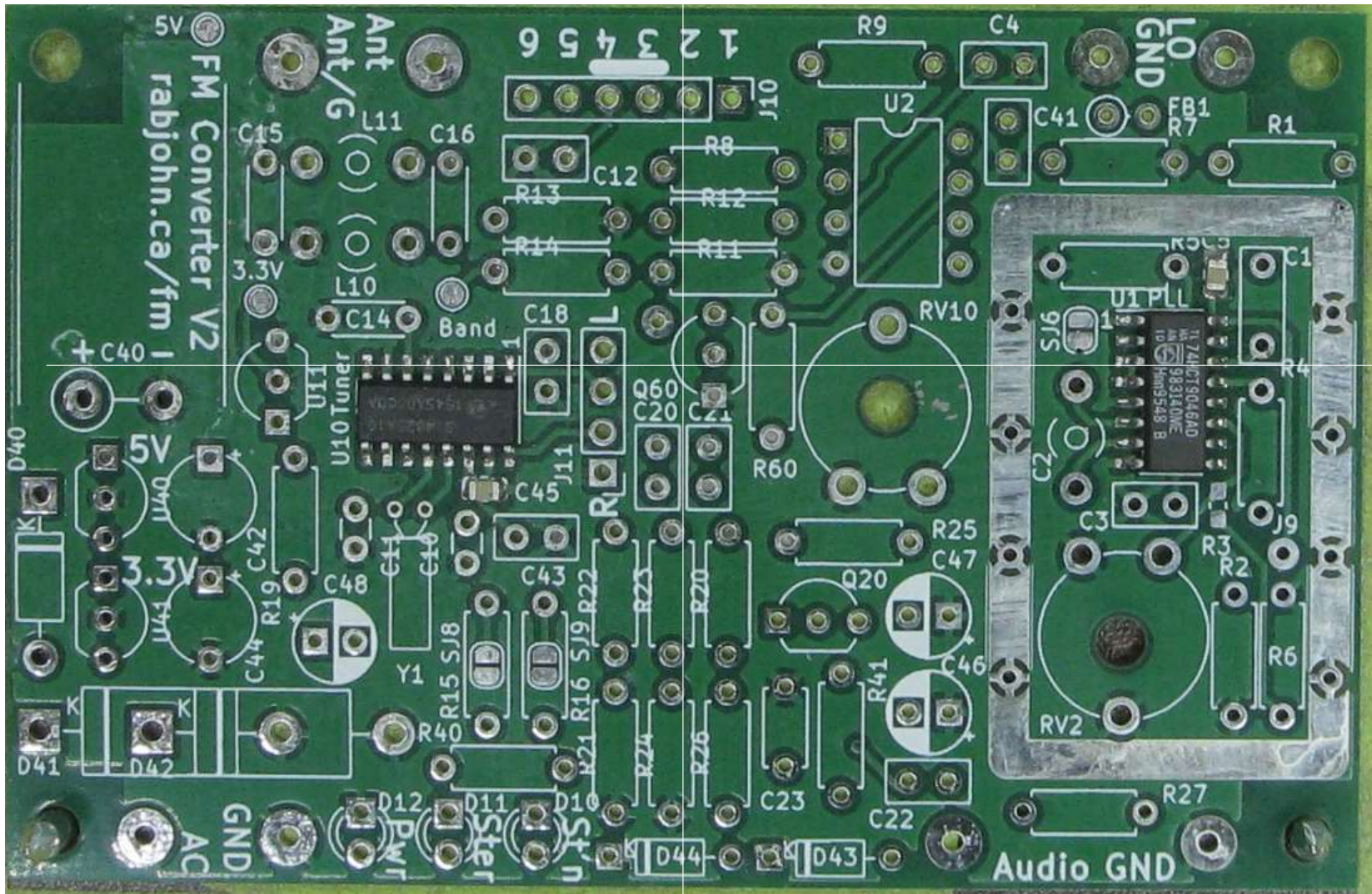

Assembly Instructions. 2. Power Supply

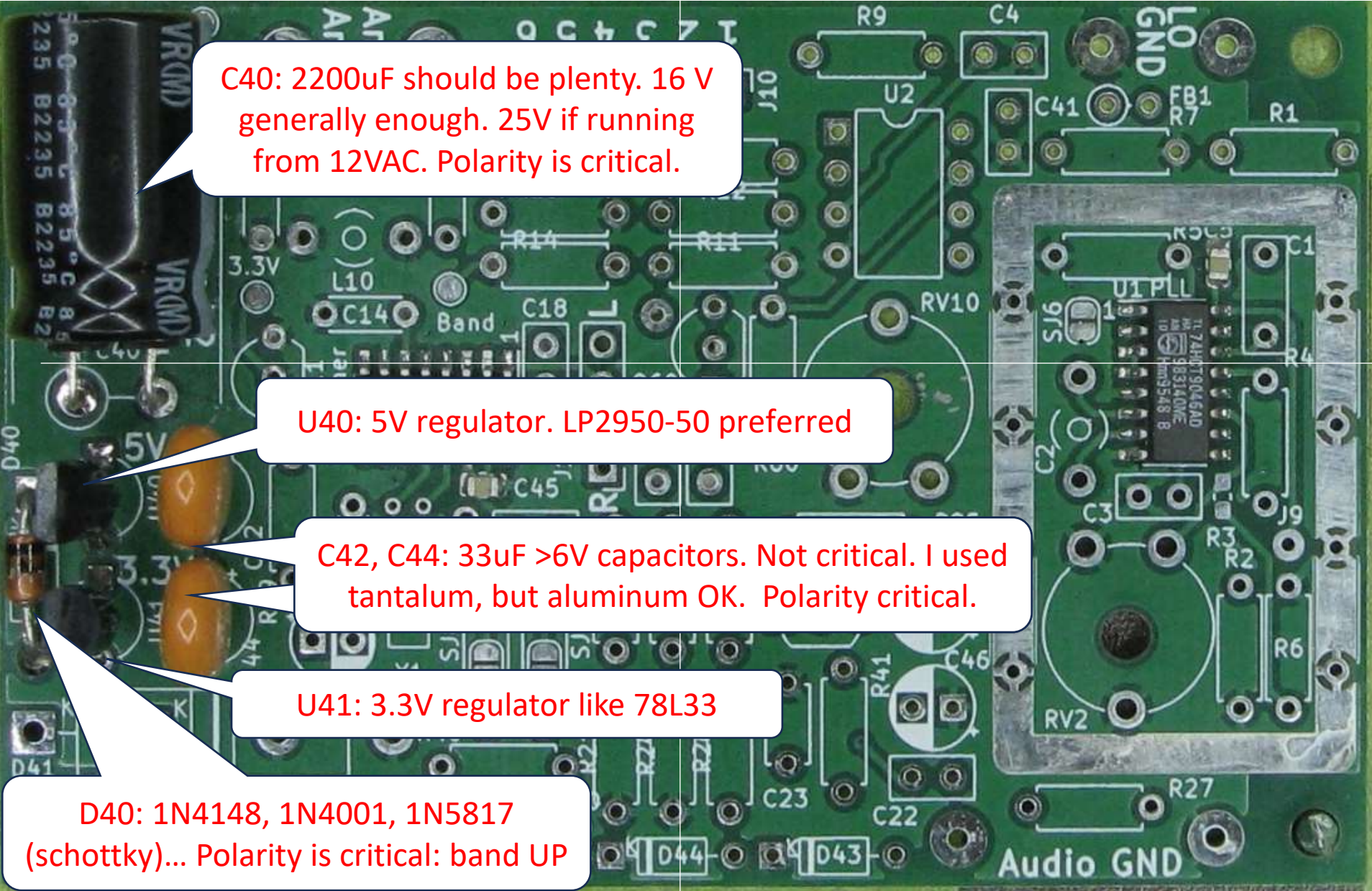

C40: 2200uF should be plenty. 16 V generally enough. 25V if running from 12VAC. Polarity is critical.


U40: 5V regulator. LP2950-50 preferred

C42, C44: 33uF >6V capacitors. Not critical. I used tantalum, but aluminum OK. Polarity critical.

U41: 3.3V regulator like 78L33


D40: 1N4148, 1N4001, 1N5817 (schottky)... Polarity is critical: band UP

Assembly Instructions. 2. Power Supply

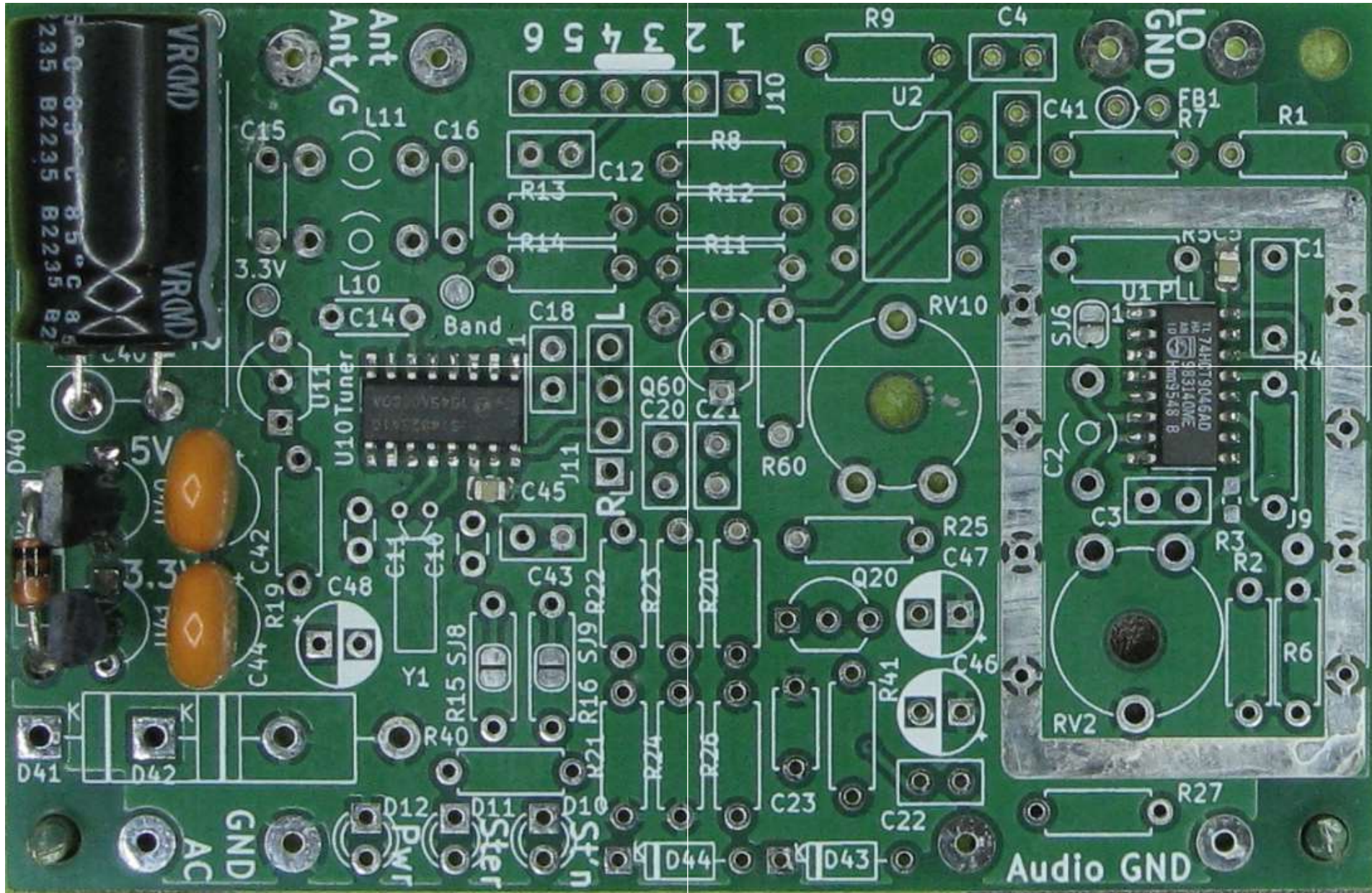

You can test the power supply. (3.3V & 5.0V)

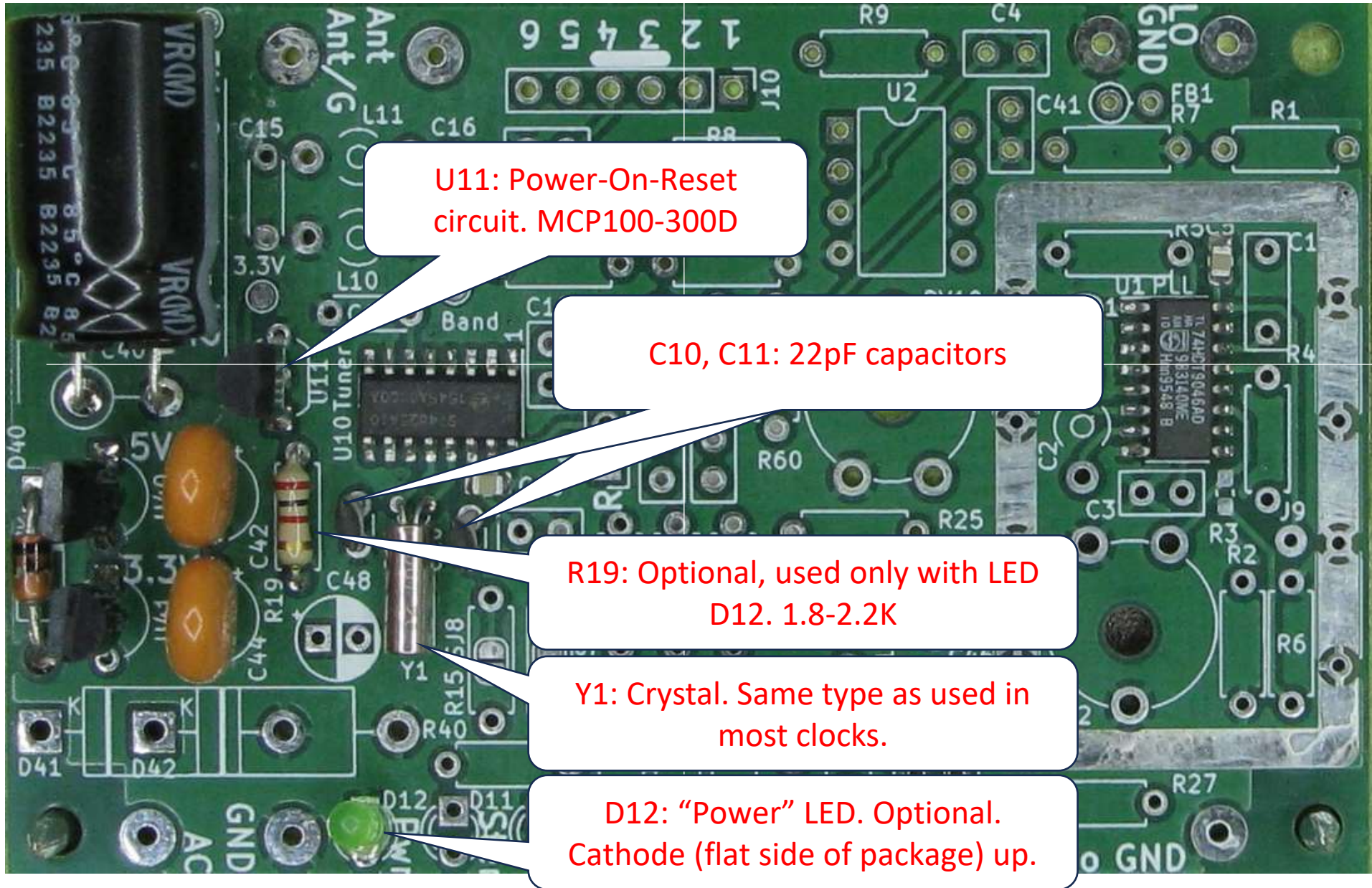Assembly Instructions. 3. Parts surrounding FM tuner



U11: Power-On-Reset circuit. MCP100-300D


C10, C11: 22pF capacitors

R19: Optional, used only with LED D12. 1.8-2.2K


Y1: Crystal. Same type as used in most clocks.

D12: "Power" LED. Optional. Cathode (flat side of package) up.

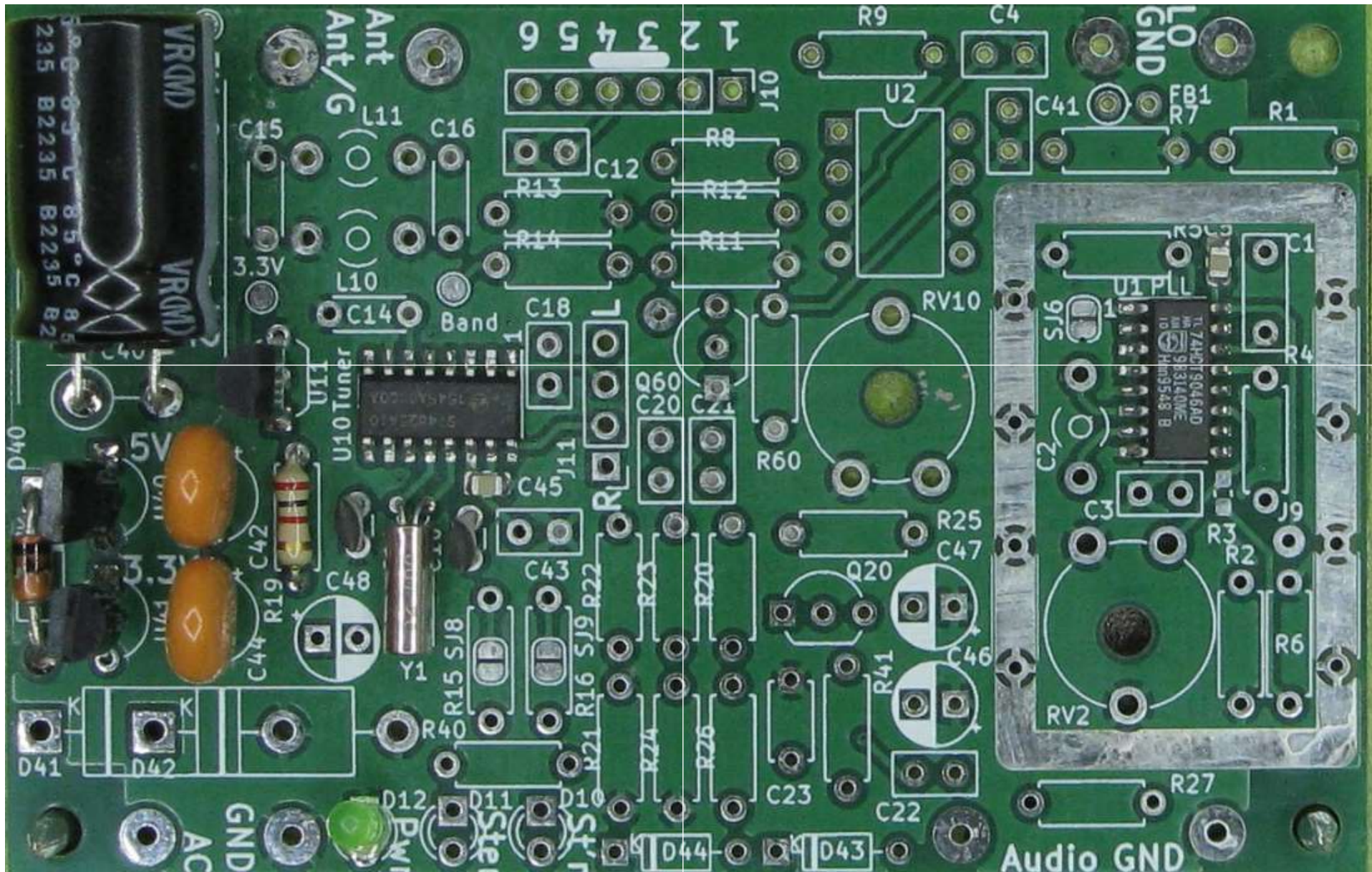Assembly Instructions. 3. Parts surrounding FM tuner




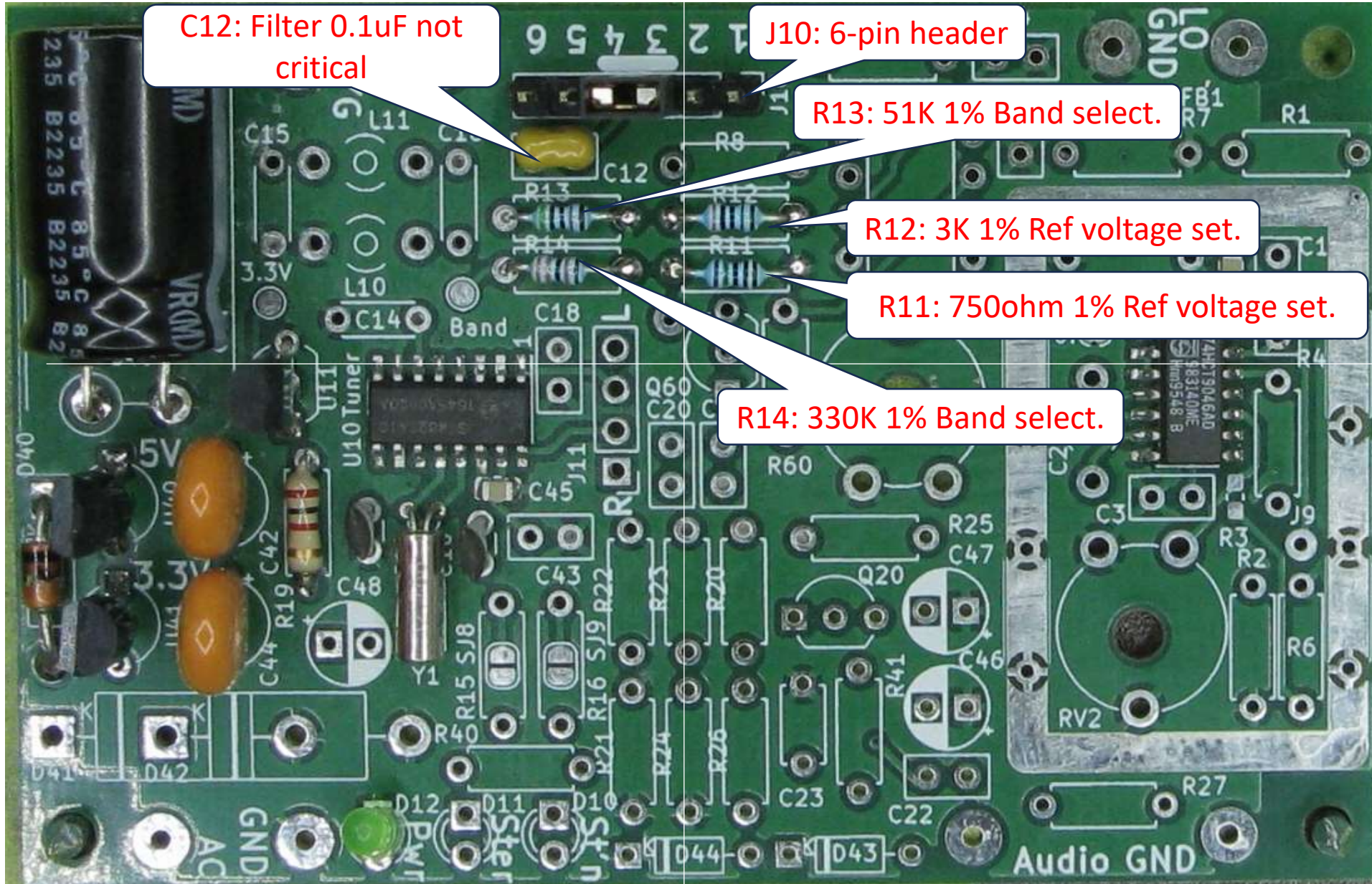Assembly Instructions. 4. Parts surrounding FM tuner




R13, R14 select the band of operation, and deemphasis options. See Si4825/4836 data sheet and application data for other band options.

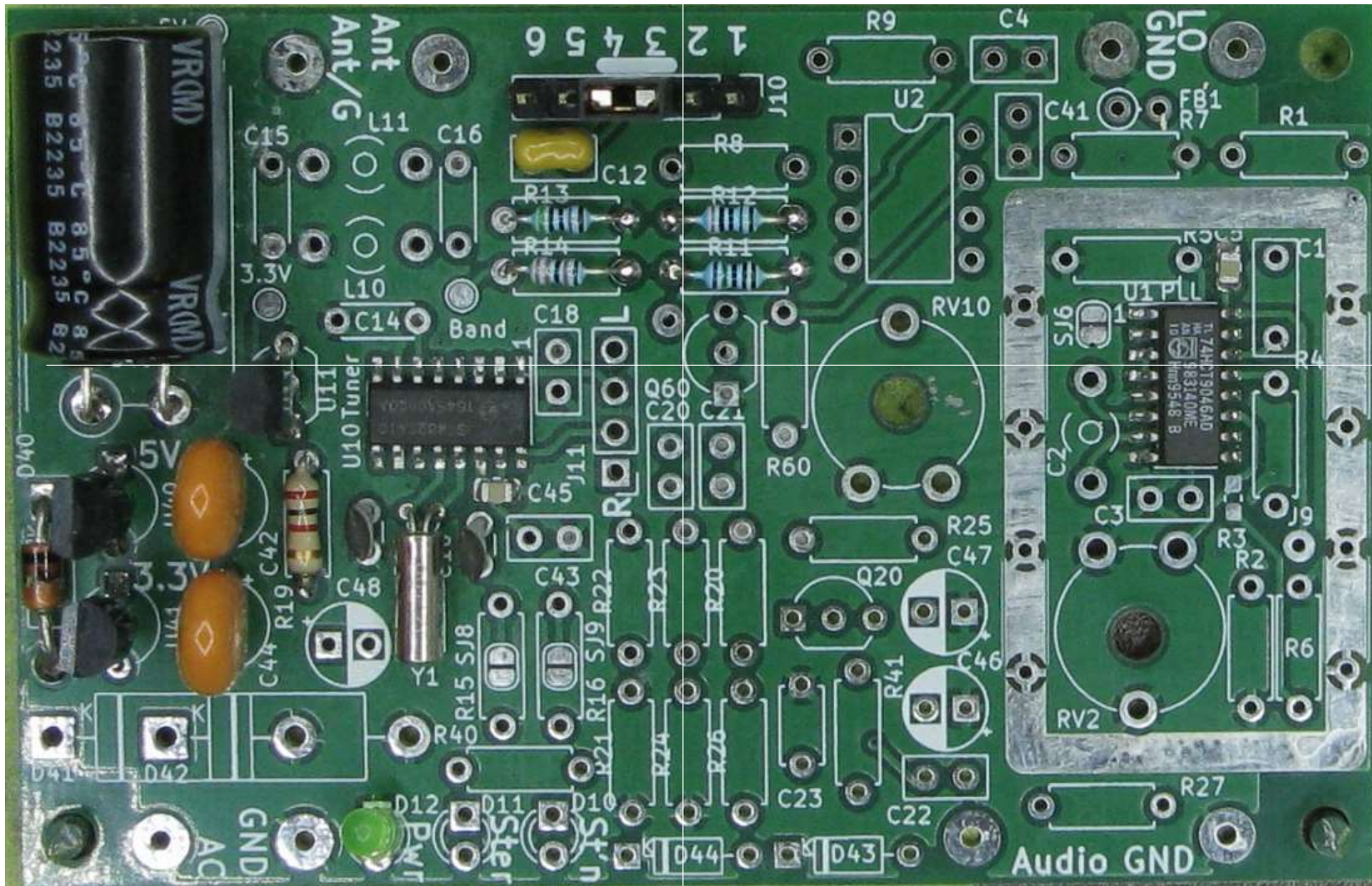
Assembly Instructions. 4. Parts surrounding FM tuner



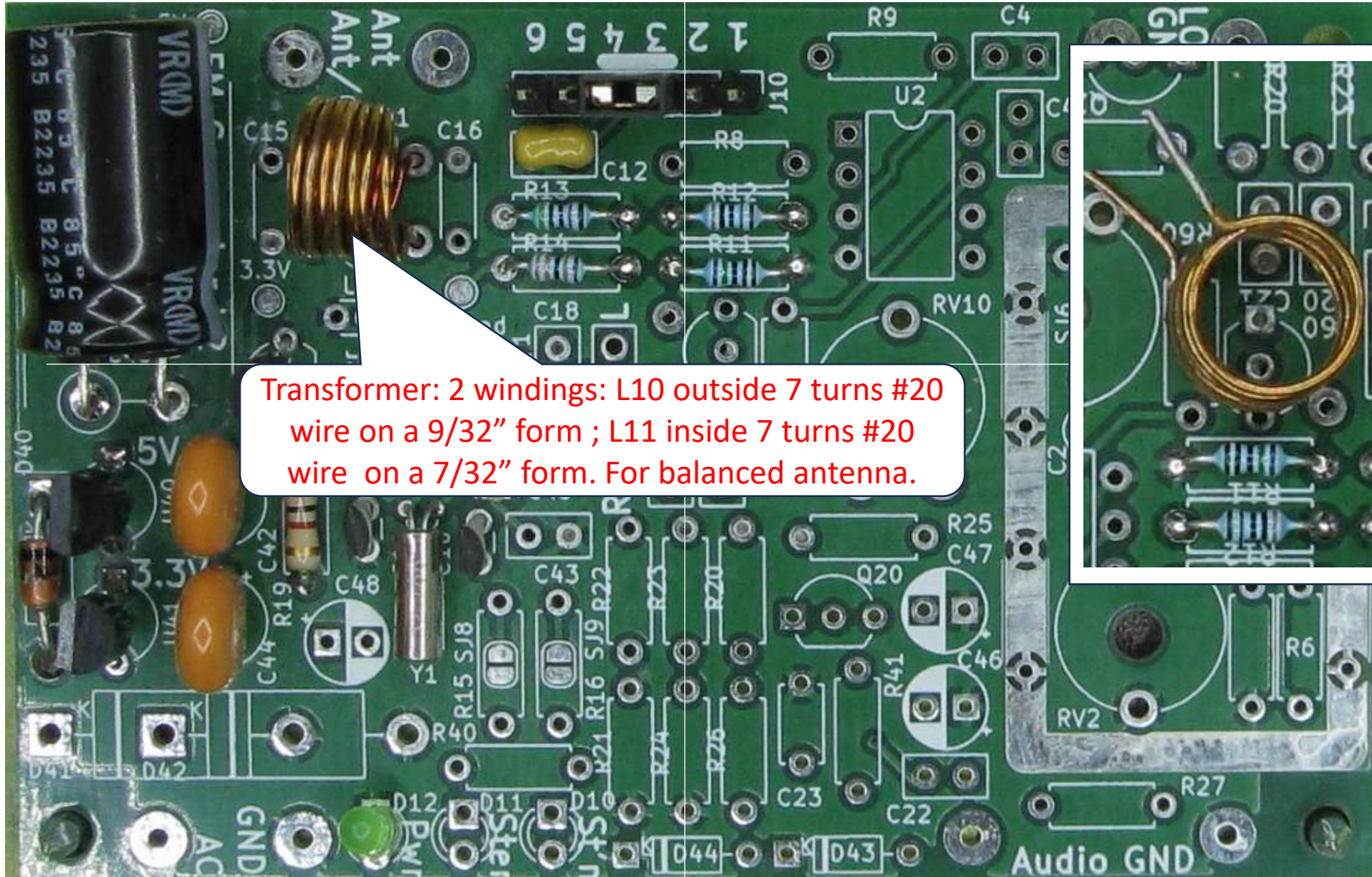
Assembly Instructions. 5a Transformer Antenna Circuit (for balanced antenna)



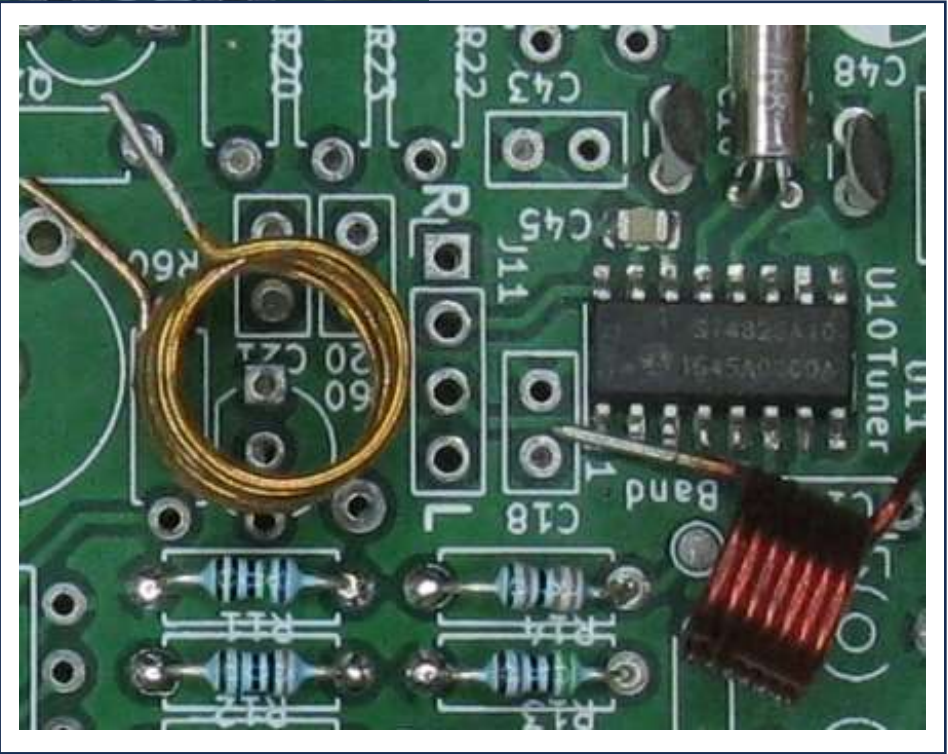Transformer: 2 windings: L10 outside 7 turns #20 wire on a 9/32" form ; L11 inside 7 turns #20 wire on a 7/32" form. For balanced antenna.



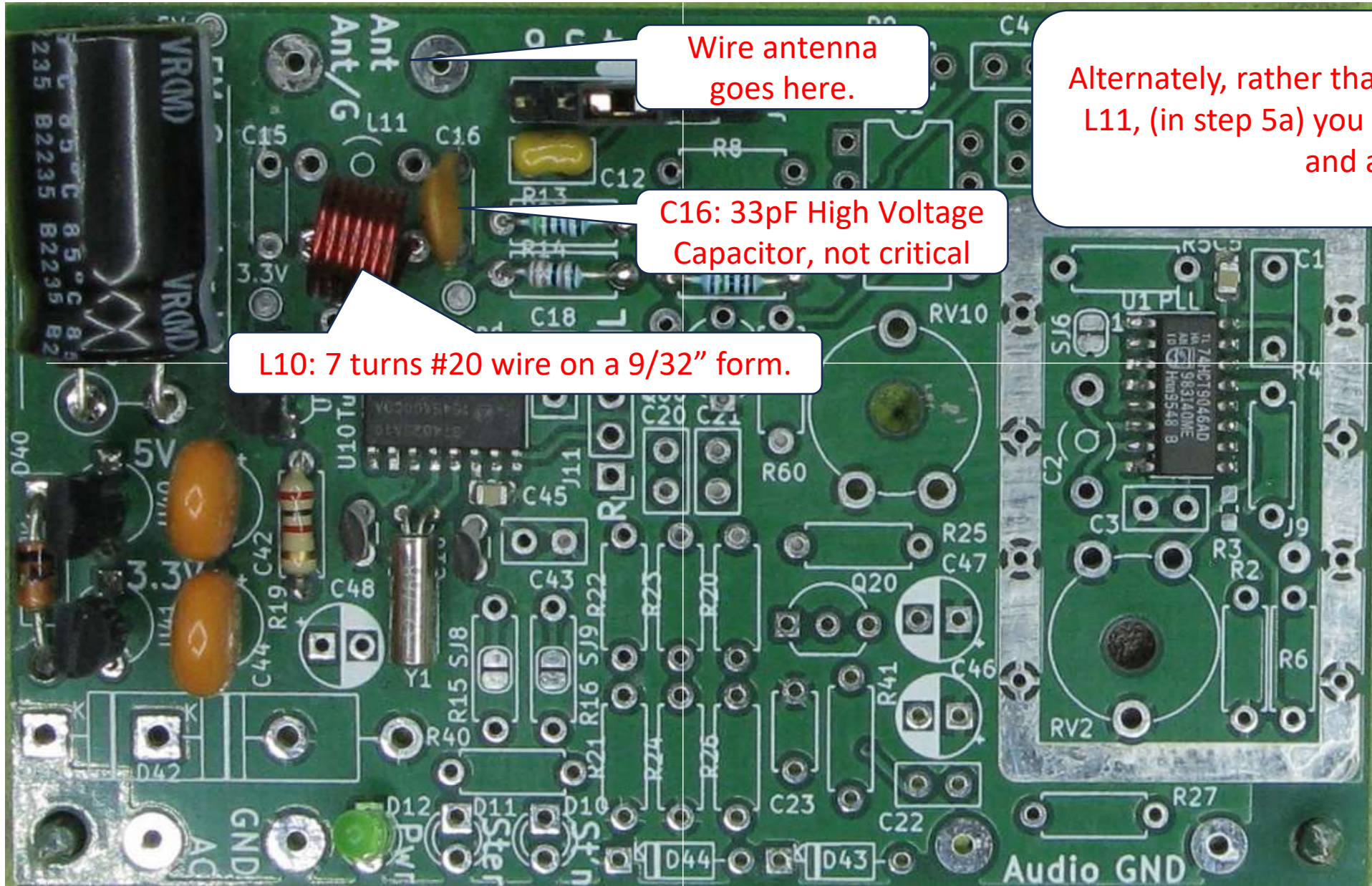Assembly Instructions. 5b L-C Antenna Circuit (for whip antenna)




Wire antenna goes here.

C16: 33pF High Voltage Capacitor, not critical

L10: 7 turns #20 wire on a 9/32" form.

Alternately, rather than the transformer at L10, L11, (in step 5a) you can just use a coil at L10 and add C16.

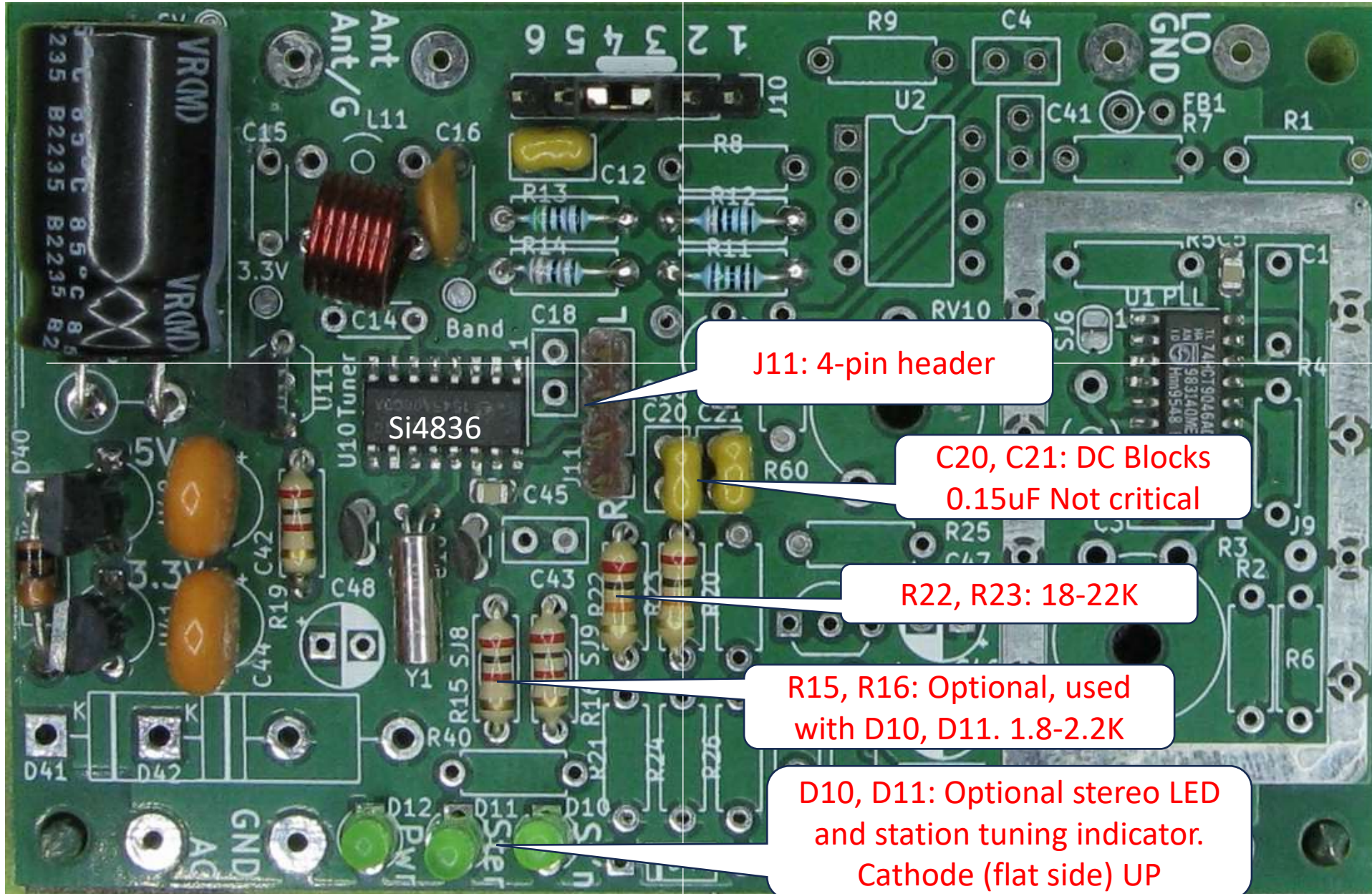Assembly Instructions. 6a. Audio Circuitry for Si4836



Si4836 ONLY

J11: 4-pin header


C20, C21: DC Blocks
0.15uF Not critical

R22, R23: 18-22K

R15, R16: Optional, used
with D10, D11. 1.8-2.2K


D10, D11: Optional stereo LED
and station tuning indicator.
Cathode (flat side) UP

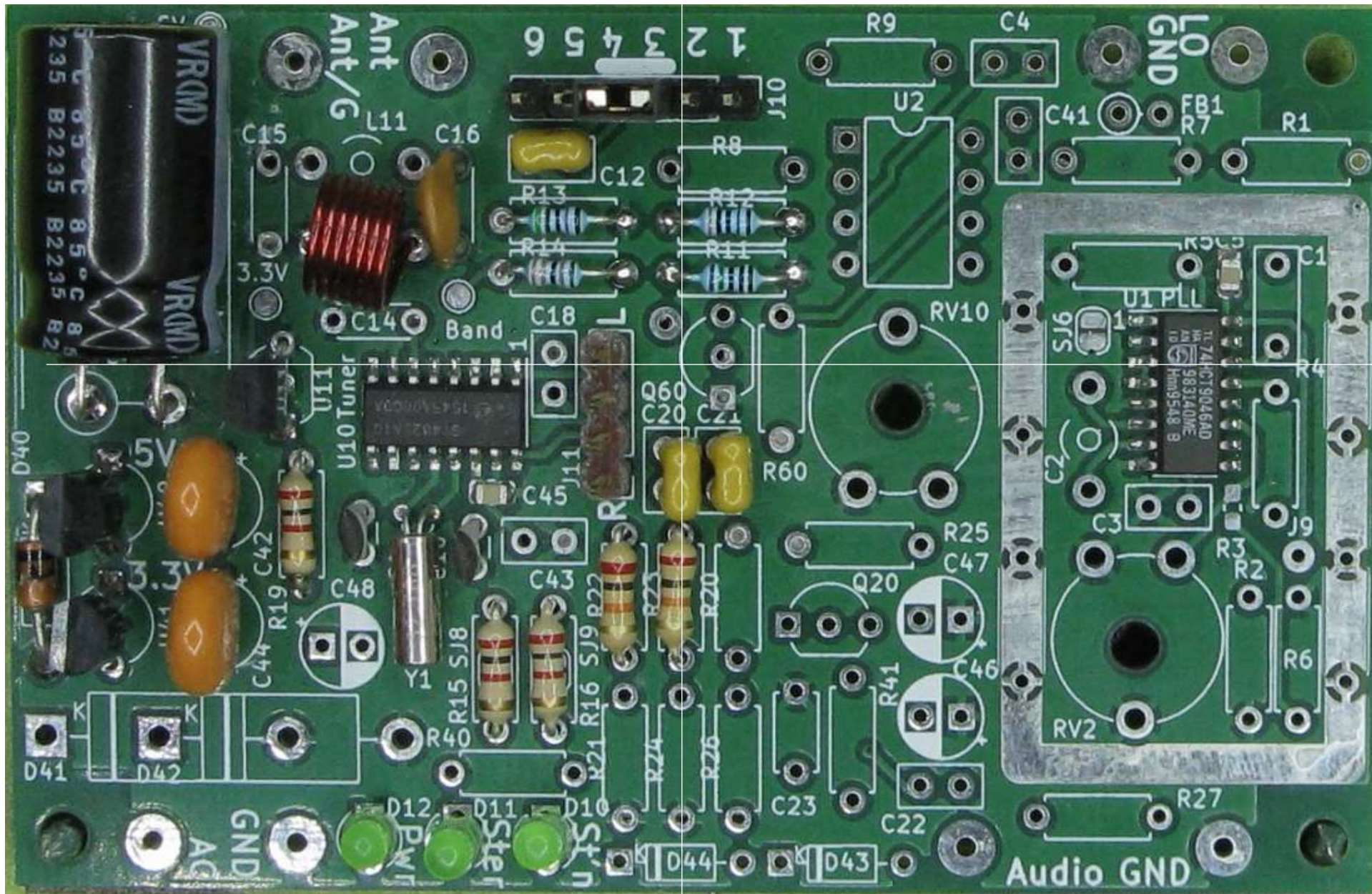Assembly Instructions. 6a. Audio Circuitry for Si4836



You can test the tuner now

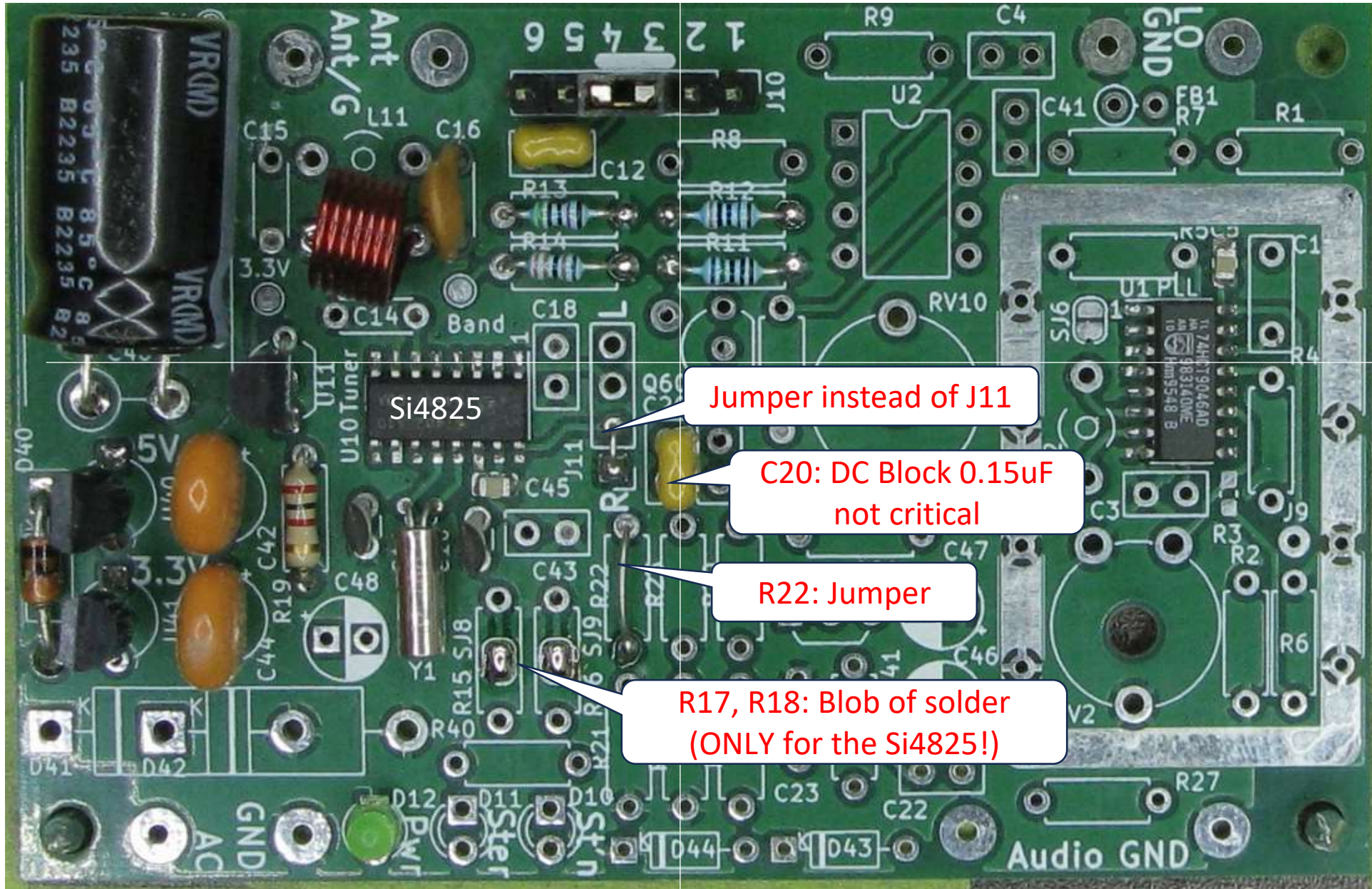Assembly Instructions. 6b. Audio Circuitry for Si4825



Si4825 ONLY


Jumper instead of J11

C20: DC Block 0.15uF
not critical

R22: Jumper


R17, R18: Blob of solder
(ONLY for the Si4825!)

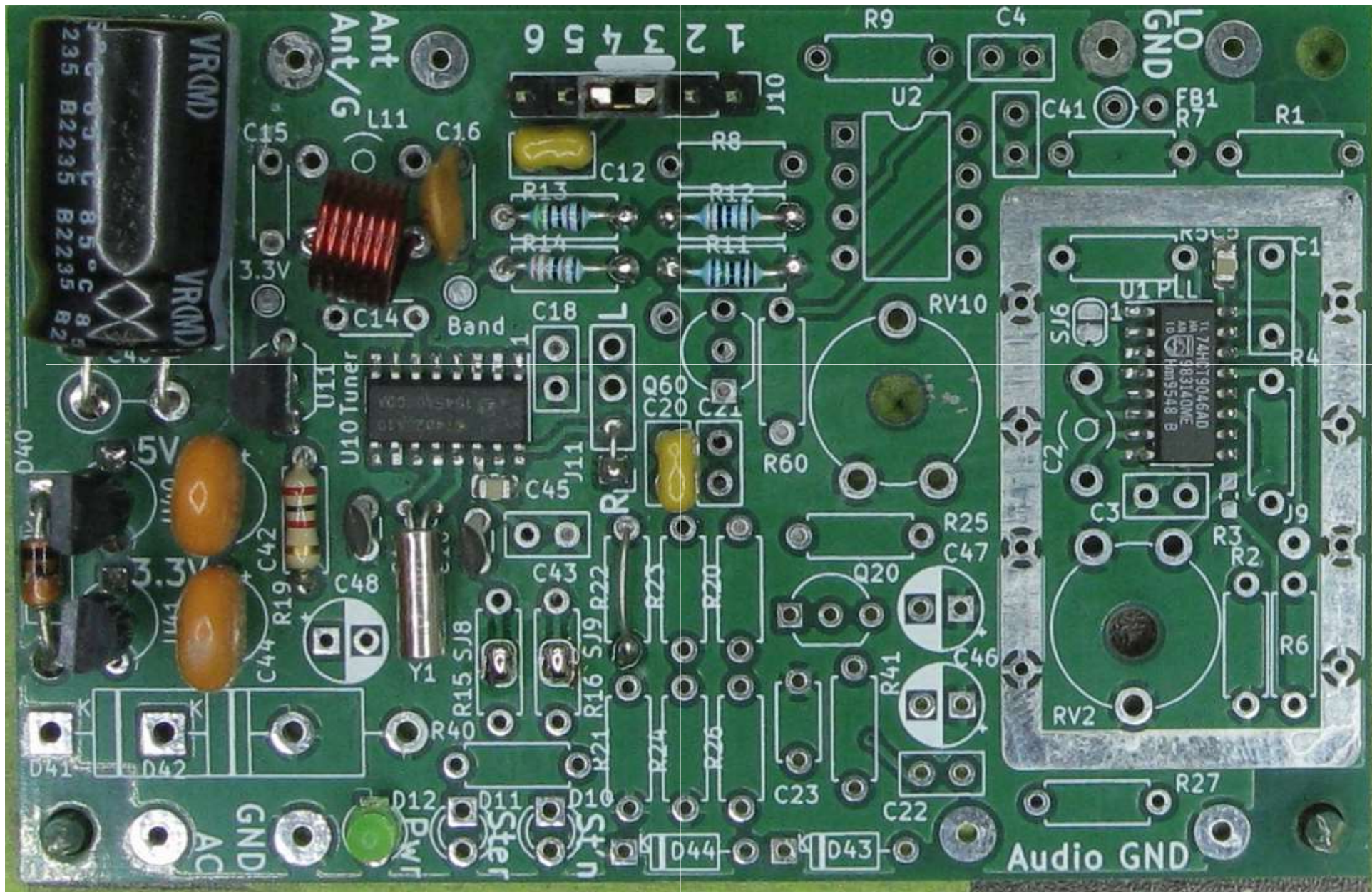Assembly Instructions. 6b. Audio Circuitry for Si4825



You can test the tuner now

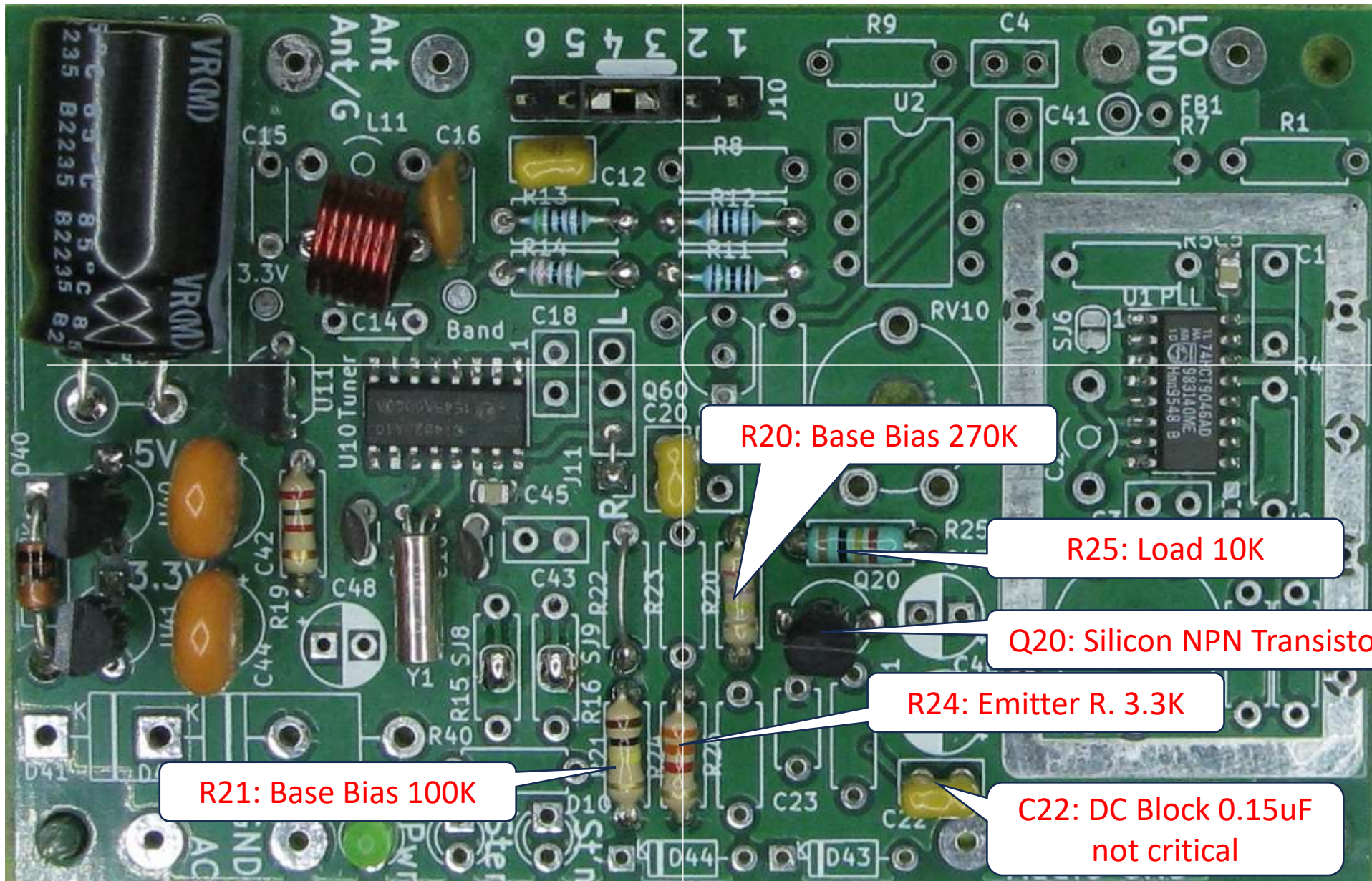Assembly Instructions. 7. Audio Amplifier



R21: Base Bias 100K

R20: Base Bias 270K


R25: Load 10K

Q20: Silicon NPN Transistor

R24: Emitter R. 3.3K


C22: DC Block 0.15uF
not critical

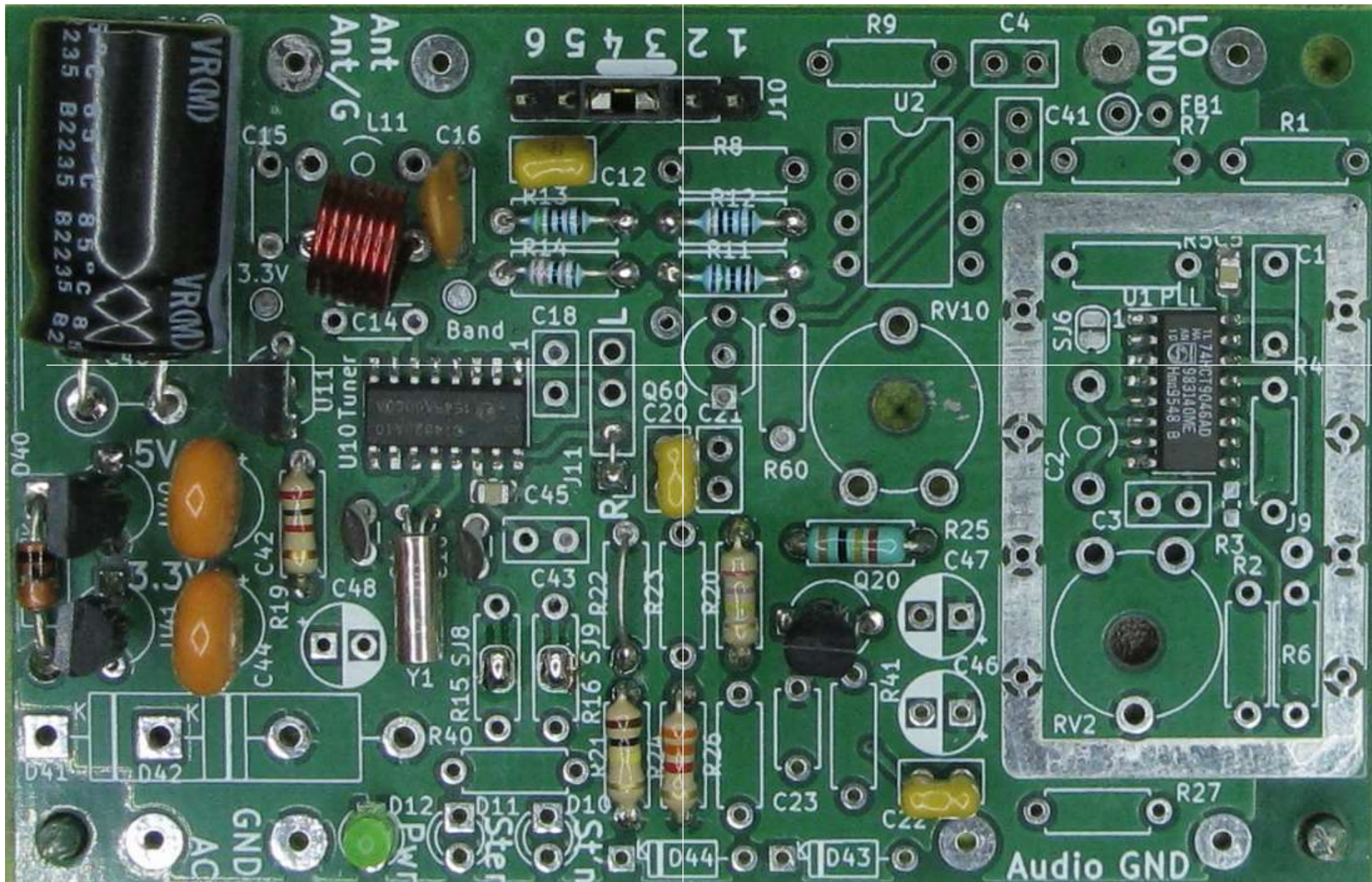Assembly Instructions. 7. Audio Amplifier



You can test the tuner + audio amplifier now

Assembly Instructions. 8. Level Shifter

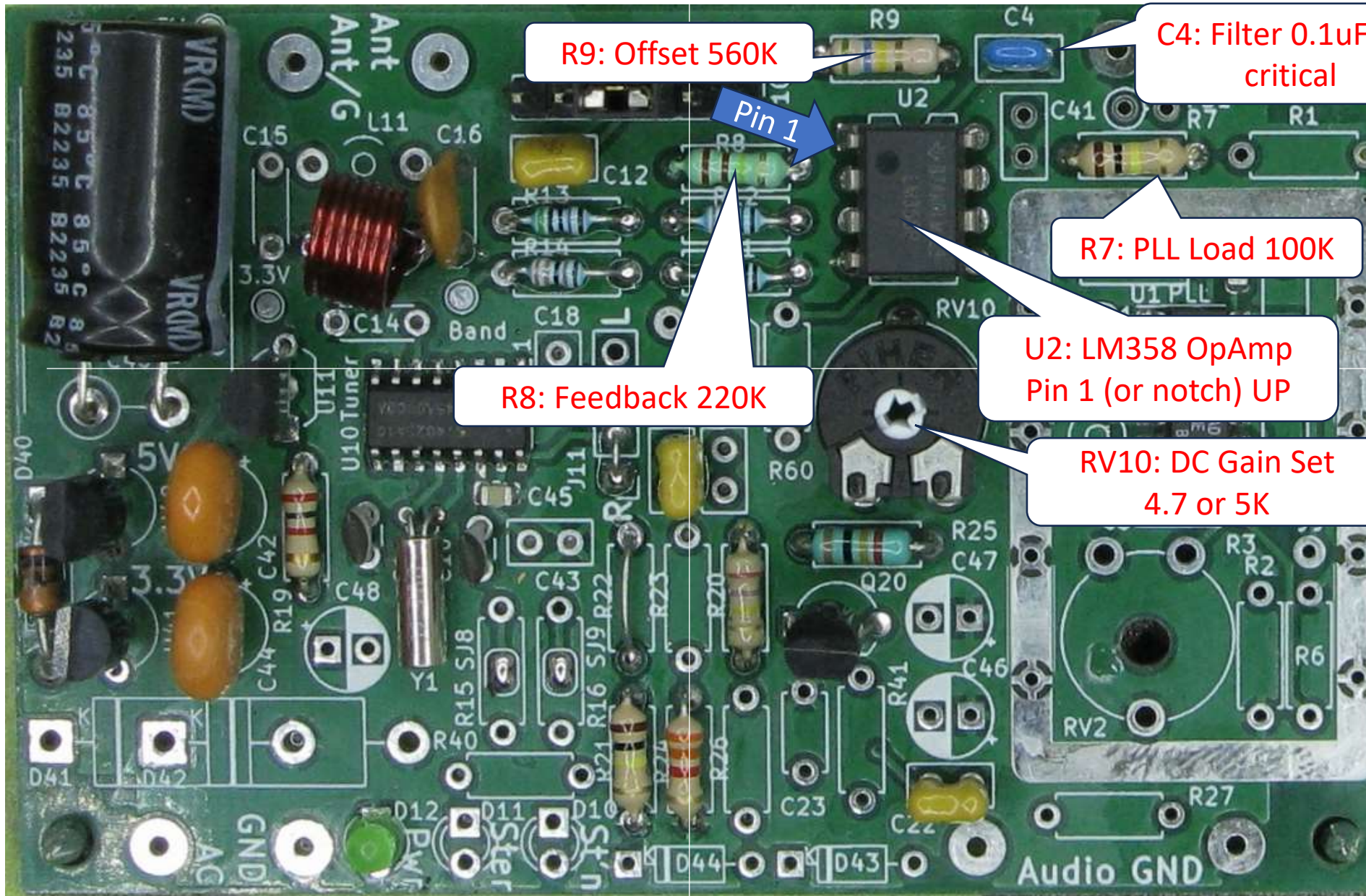

R9: Offset 560K

C4: Filter 0.1uF not critical

Pin 1


R7: PLL Load 100K

R8: Feedback 220K


U2: LM358 OpAmp
Pin 1 (or notch) UP

RV10: DC Gain Set
4.7 or 5K

Assembly Instructions. 8. Level Shifter

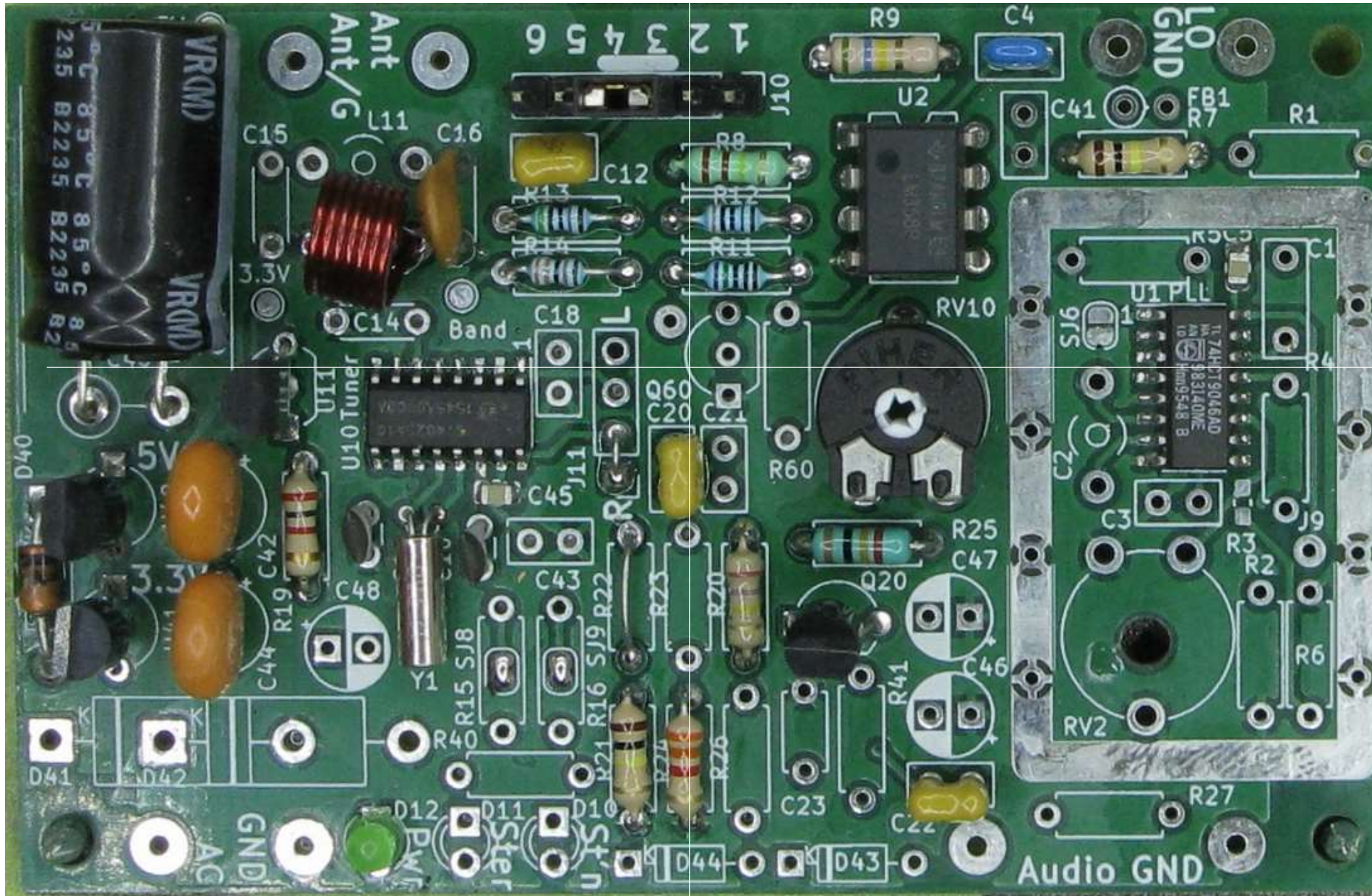

Assembly Instructions. 9. PLL

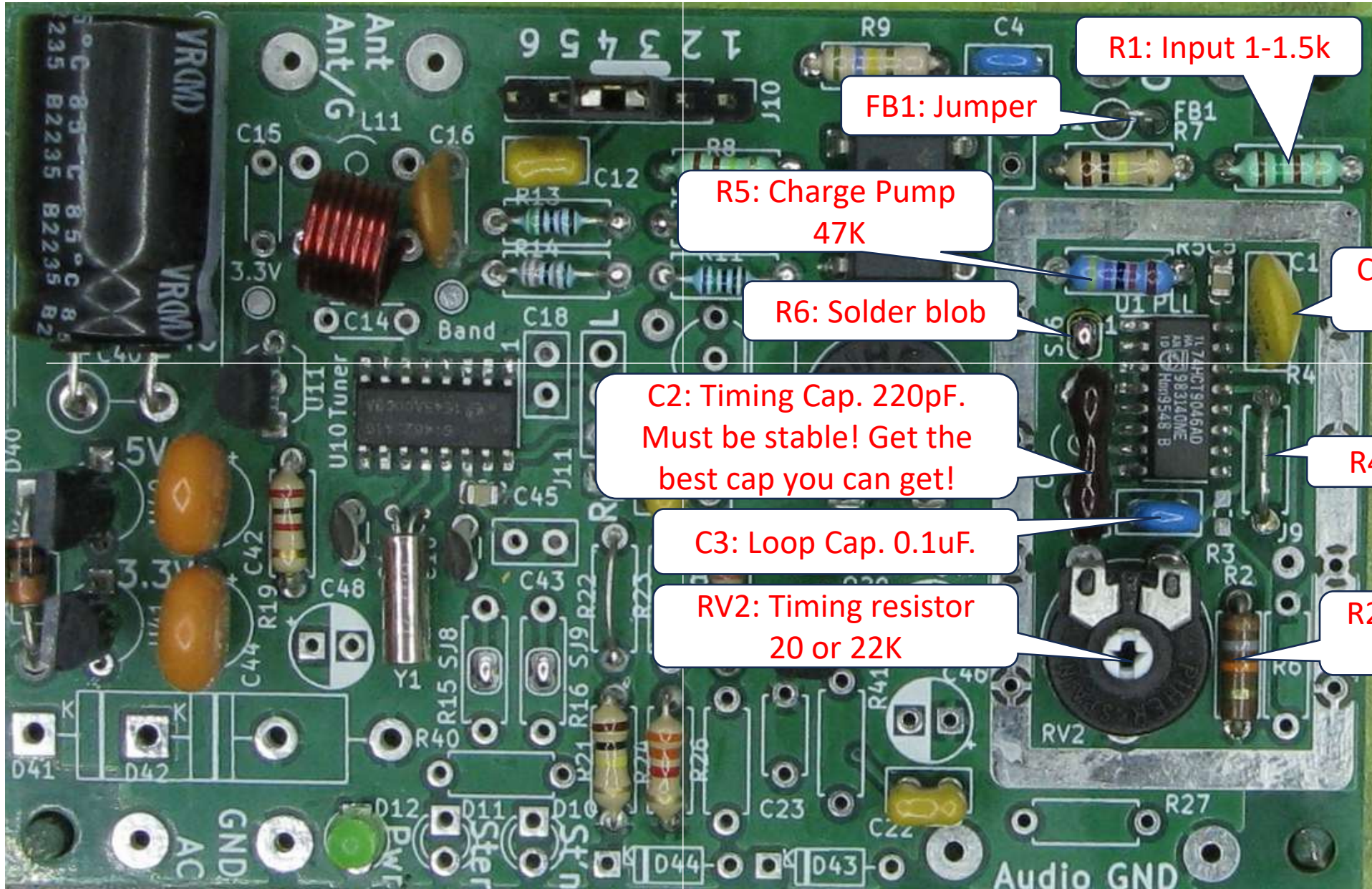

R1: Input 1-1.5k

FB1: Jumper

R5: Charge Pump
47K

R6: Solder blob

C1: LO Coupling 100pF
not critical

C2: Timing Cap. 220pF.
Must be stable! Get the
best cap you can get!


R4: Jumper

C3: Loop Cap. 0.1uF.

RV2: Timing resistor
20 or 22K


R2: Stability
18K

Assembly Instructions. 9back. PLL

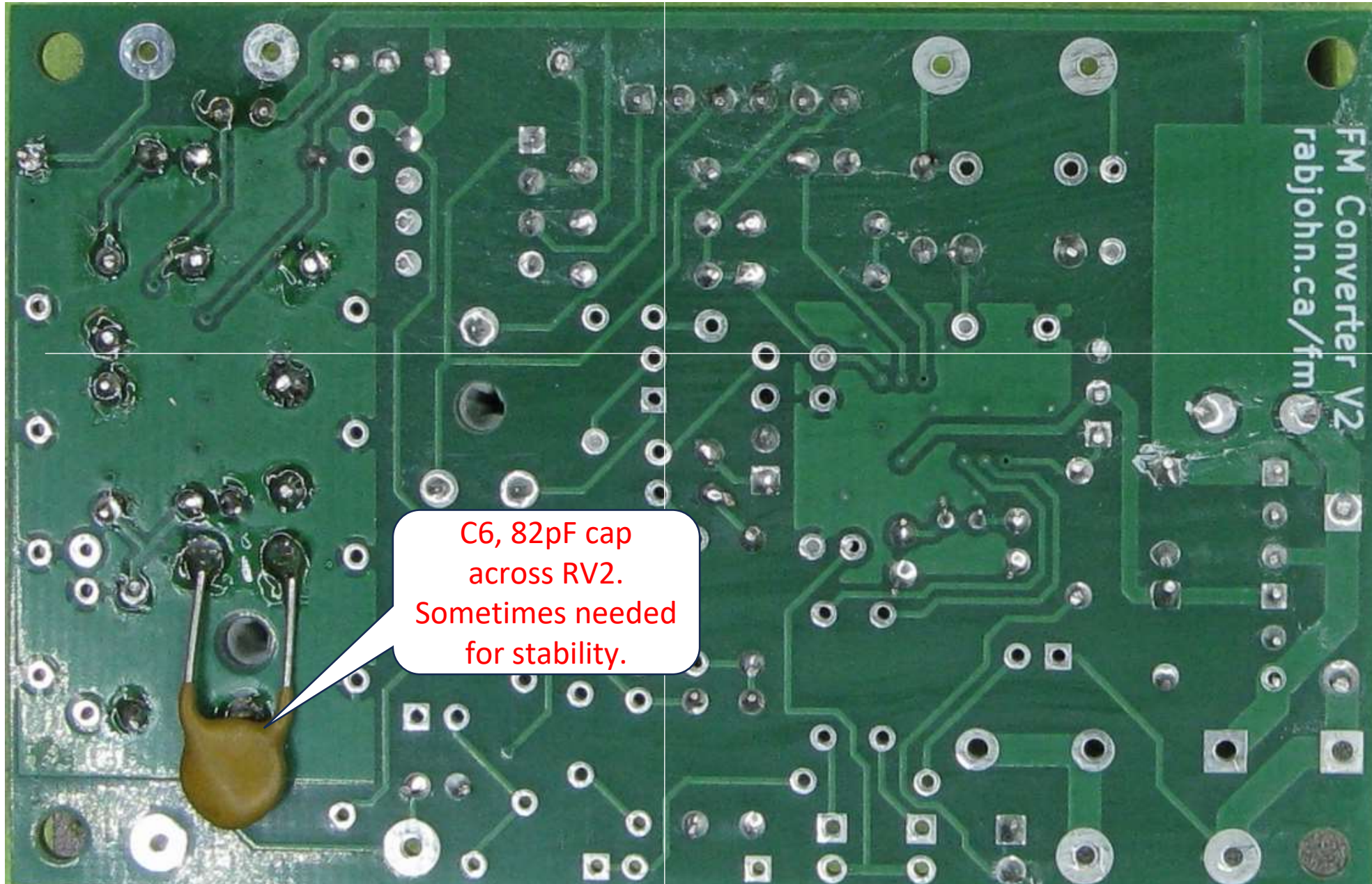

C6, 82pF cap
across RV2.
Sometimes needed
for stability.

Assembly Instructions. 9. PLL

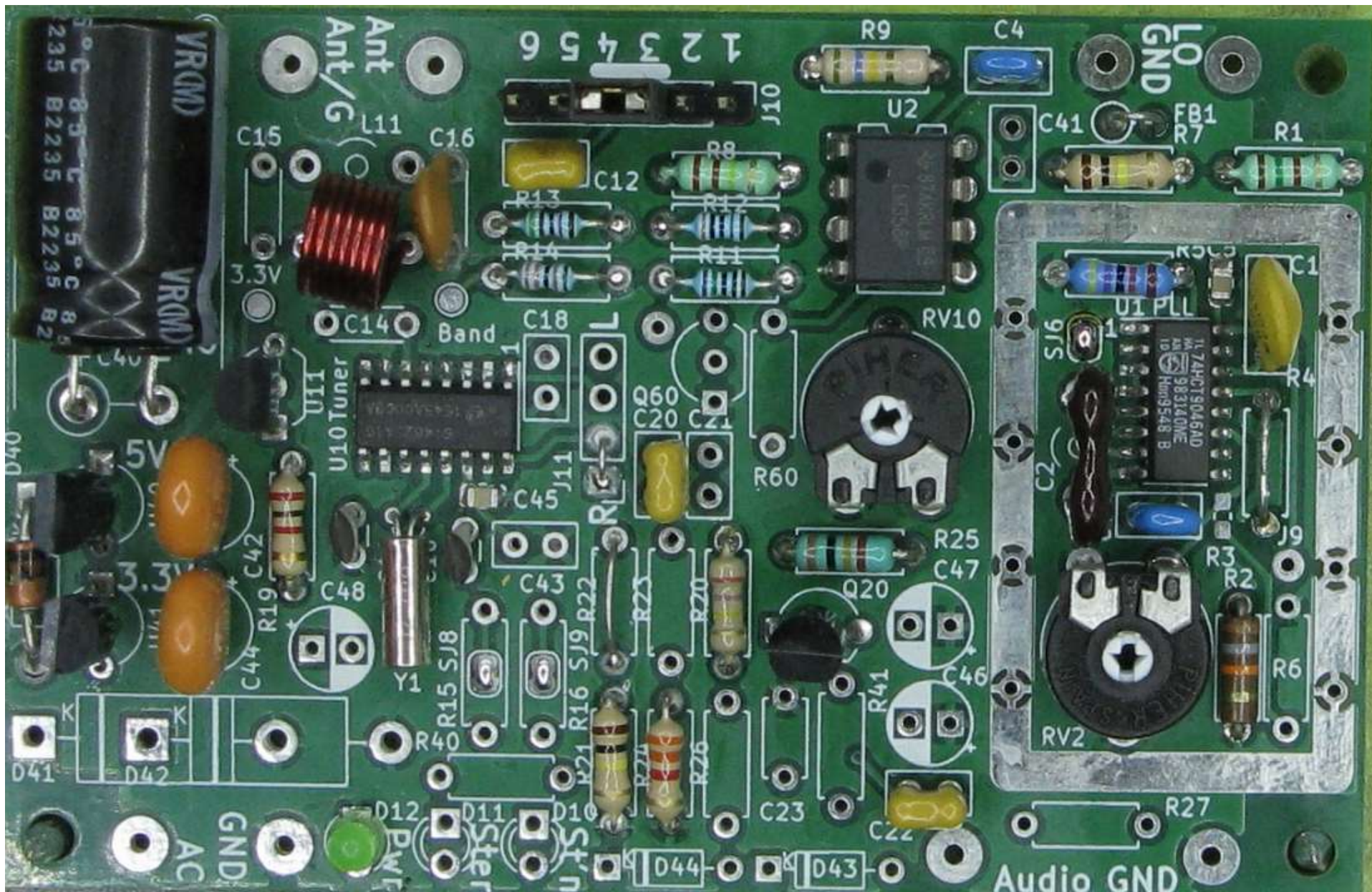


The basic converter is done. You can test it now

Negative Supply Voltage Supply

- This voltage reverse-biases the host radio's detector (deactivating it). If the detector is not deactivated (either by disconnecting it or reverse biasing it), it can cause distortion.
- The negative voltage also reduces the gain of the IF amplifier (eliminating it as a potential source of noise or AM feedthrough).
- If the detector diode is disconnected, the reverse supply is not necessary.
- In parallel filament radios, the IF amplifier tube can be removed to reduce AM feedthrough.
- In radios powered by DC (eg. car radios), the negative voltage generator does not work.
- In series heater string radios (AC-DC sets using the 8.2V Zener diode), it will generate about -7V; enough to disable the detector.

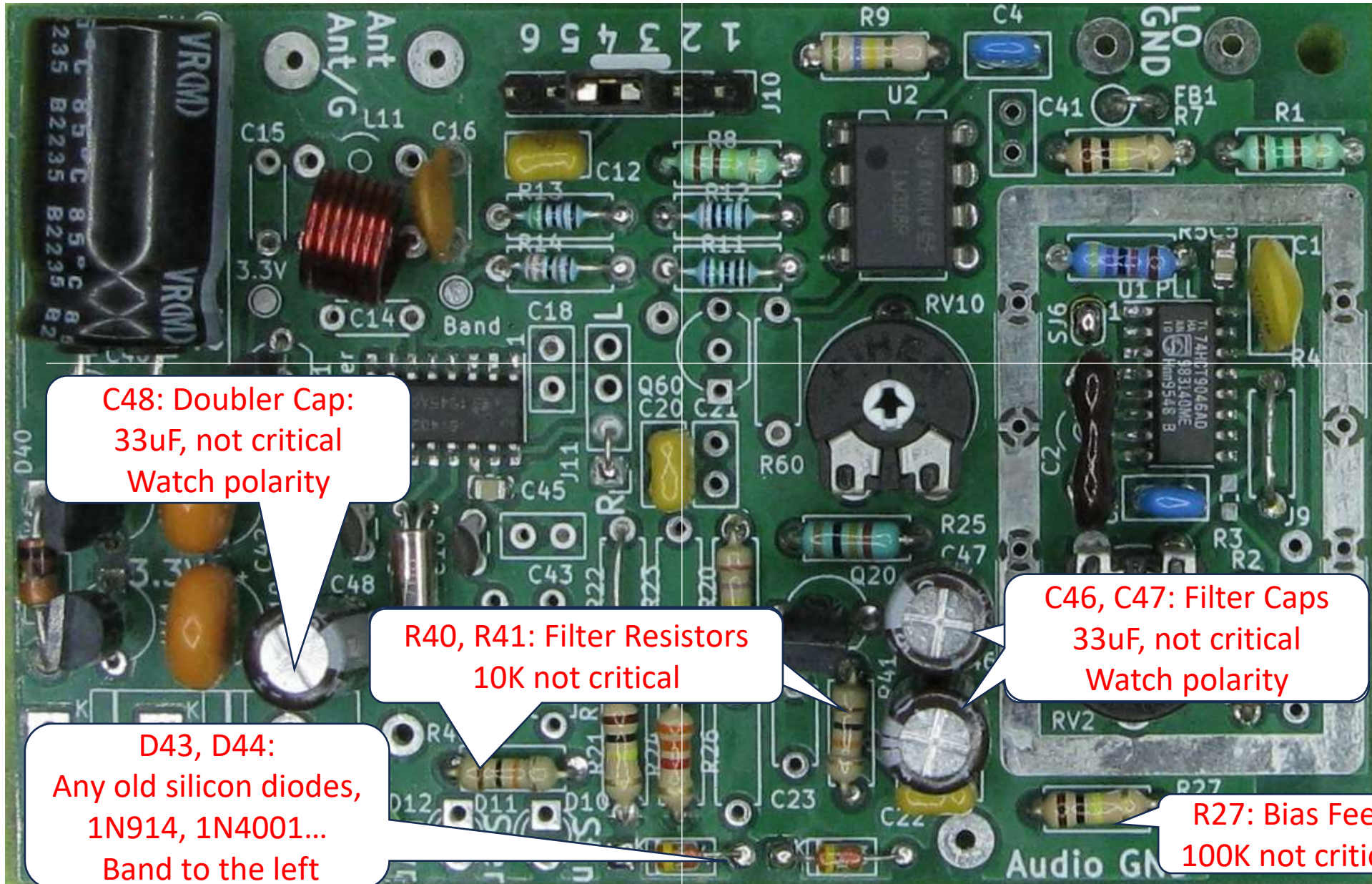Assembly Instructions. 10. Negative Supply



C48: Doubler Cap:
33uF, not critical
Watch polarity


R40, R41: Filter Resistors
10K not critical

D43, D44:
Any old silicon diodes,
1N914, 1N4001...
Band to the left

C46, C47: Filter Caps
33uF, not critical
Watch polarity

R27: Bias Feed
100K not critical


Here's a board made with the Si4836

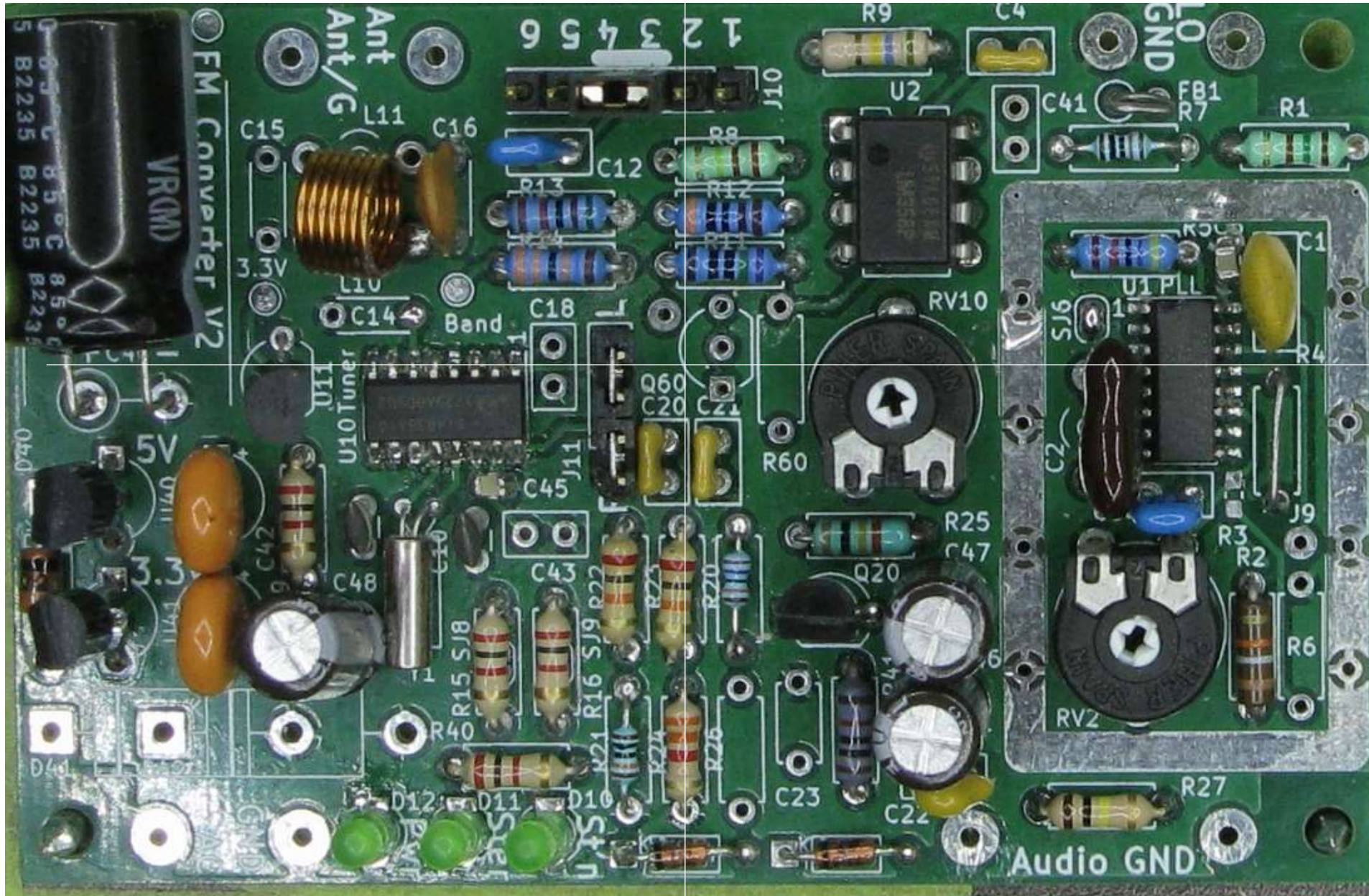

Protection Diodes

- In series heater radios, where the FMC is powered in series with the heaters, an 8.2V Zener diode is used at D41. This carries the 150mA (typical) heater current, and limits the voltage into the converter to 8.2V.
- *D41 is absolutely necessary for series-string operation.*
- In series heater radios, where the converter is powered in parallel with one of the heaters (recommended only with 300mA series string), a Zener diode (10V -20V, high enough that it is not on) is used at D42. This diode is usually off, but if the heater opens, it prevents the converter from getting damaged by excess voltage.
- In parallel heater radios, no protection diode is required.

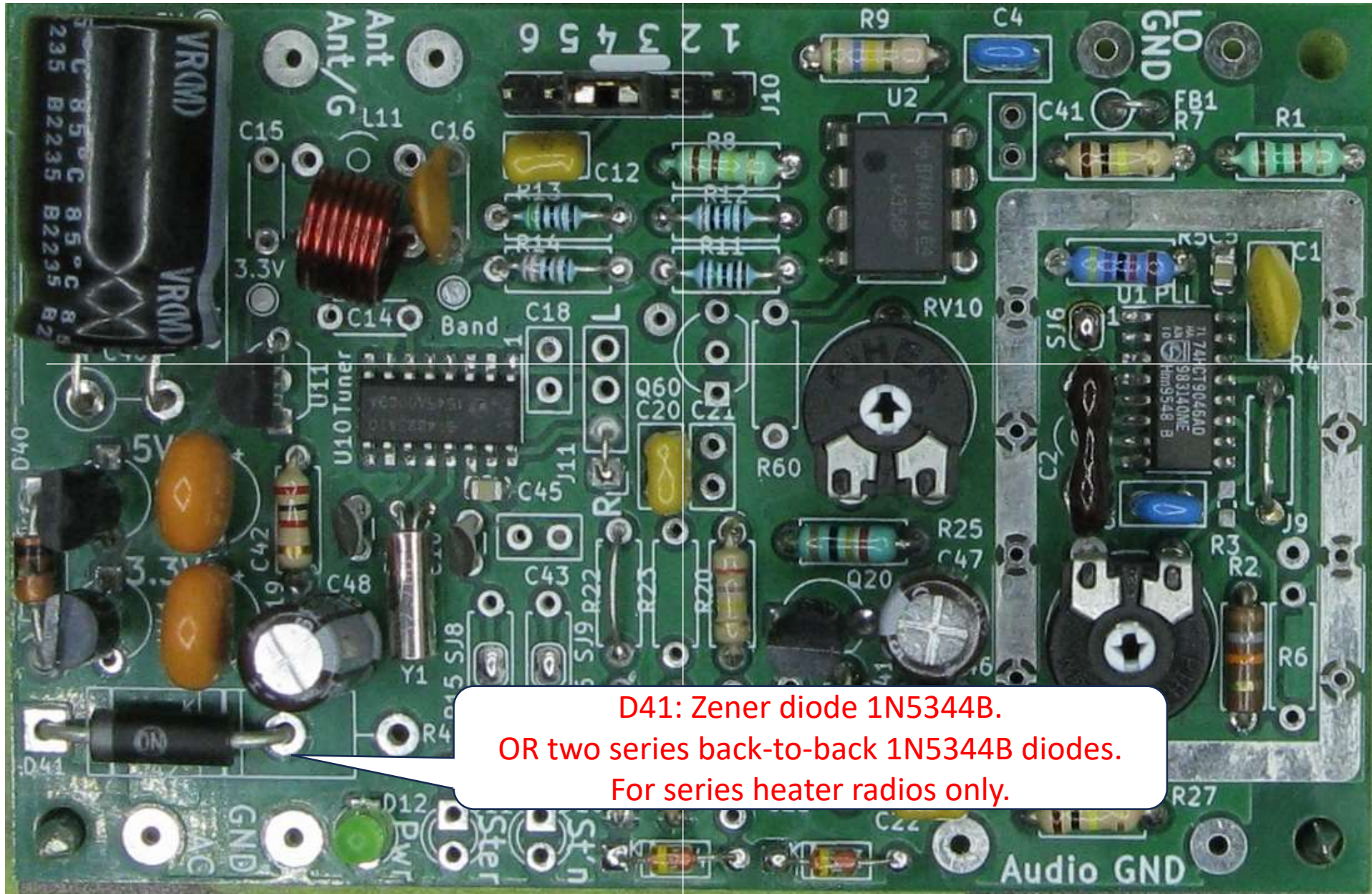Assembly Instructions. 11A. Protection (D41)



D41: Zener diode 1N5344B.
OR two series back-to-back 1N5344B diodes.
For series heater radios only.

Tests

DC Tests

Measure 5V

Vref:
Measure 1V


Band Select:
Measure 0.134V

Measure 3.3V

Measure ~ 3V


Measure ~ -16V (when
supplied from 6.3VAC)

Apply
6VAC

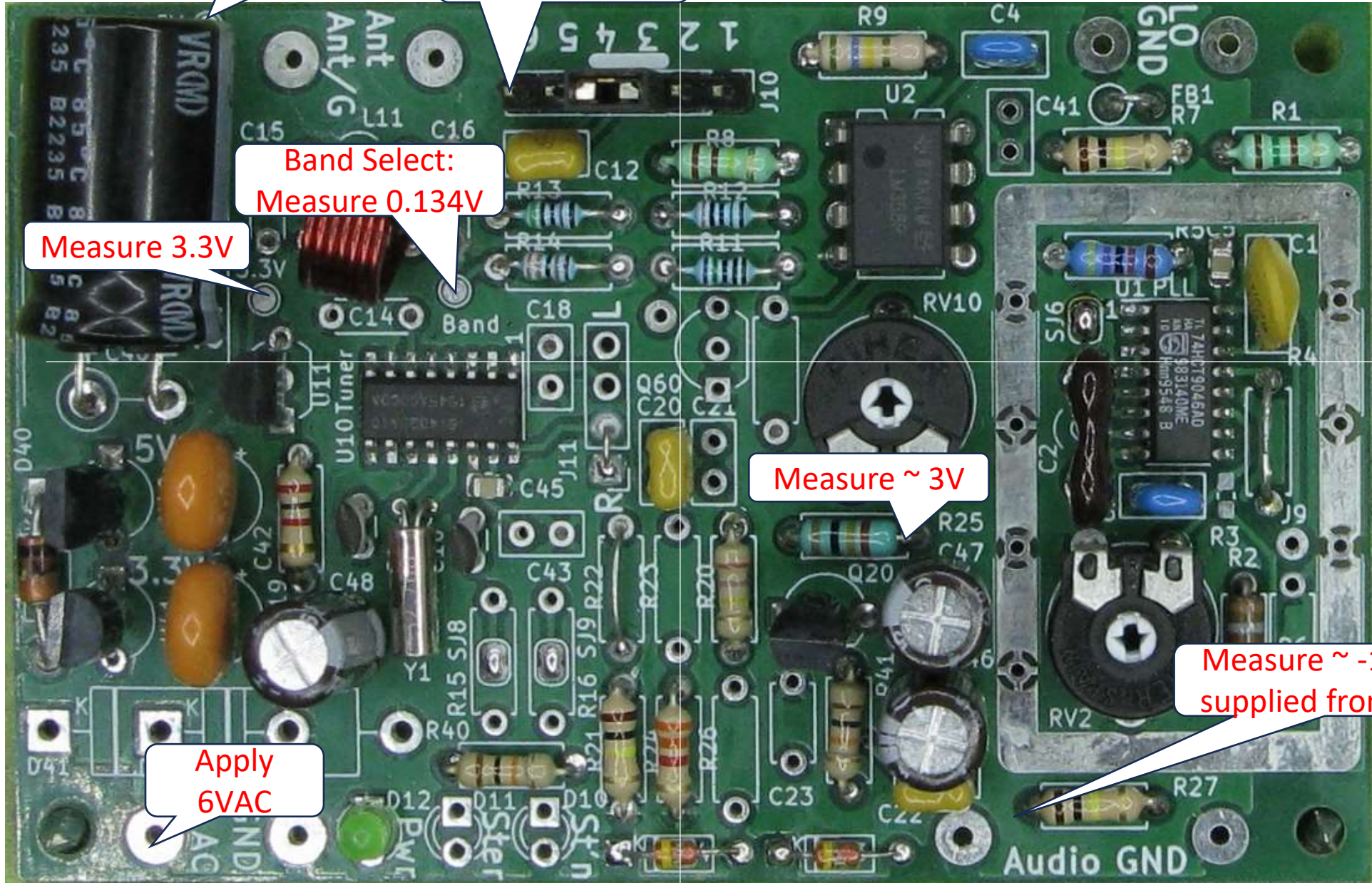

Full Test (after PLL adjustment) 1m antenna wire

To an adjustable, stable RF source 1MHz to 2MHz

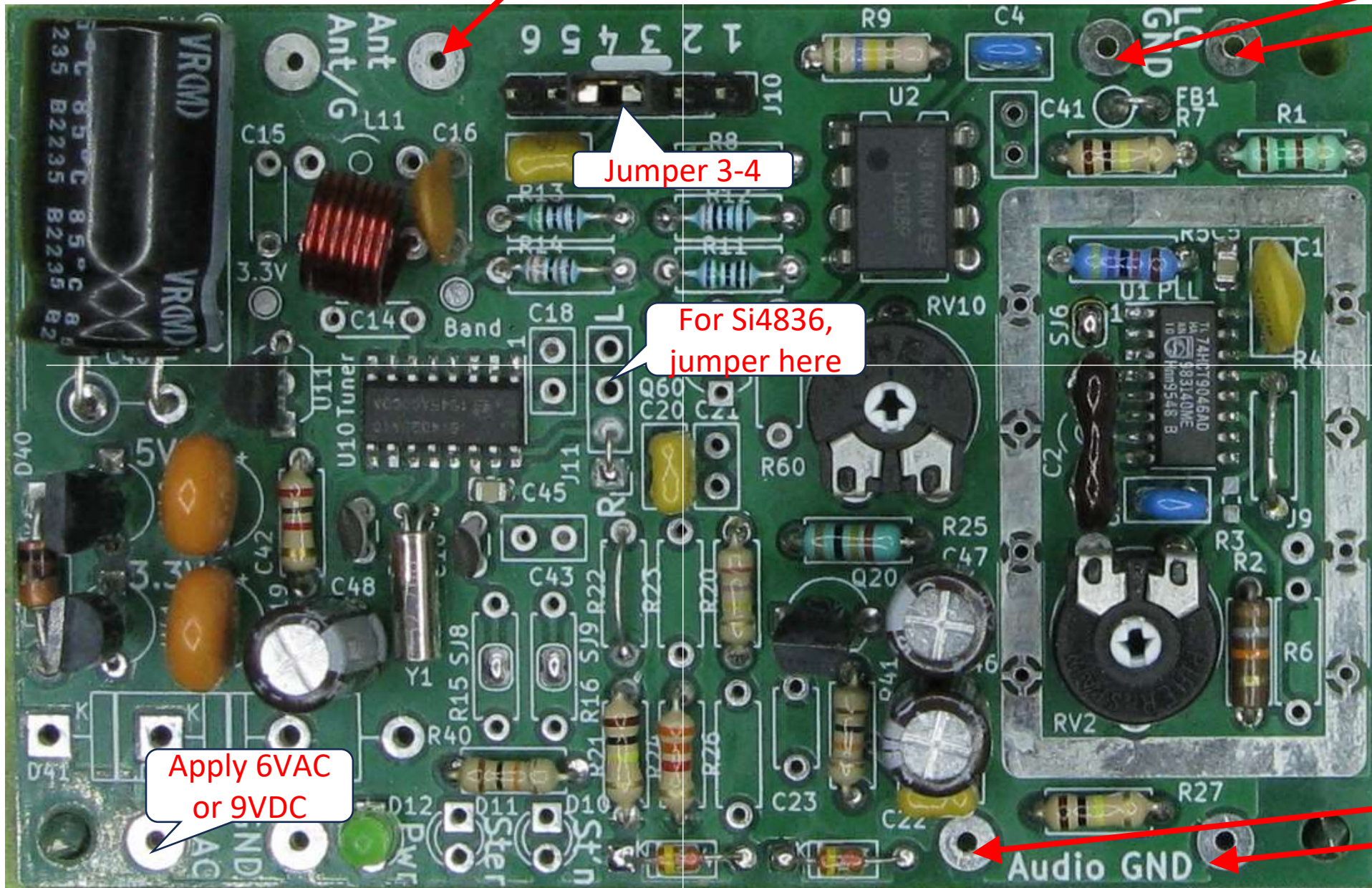

Jumper 3-4

For Si4836, jumper here

Apply 6VAC or 9VDC

Audio GND

Connect the RF source, audio amp, antenna, power supply (or a 9V battery works).

Jumper J10 from pin 3 to 4. If you use a Si4836 chip, jumper pins 1 to 2 and 3 to 4 on J11

As the RF source is adjusted from 1MHz to 2MHz, stations across the full FM band should be heard.

To an audio amplifier

Alignment

- Jumper J10 pin 3 to 4. If you use a Si4836, jumper J11 pins 1 to 2 and 3 to 4
- Connect board to radio as described in the FM_conversion_ACset or FM_conversion_AA5 or FM_conversion_car radio
- Connect a DC voltmeter from J10 pin 4 to pin 2 (ground).
- You might need an antenna, a metre of wire.
- Turn on radio and let it warm up. Rotate RV10 fully clockwise, RV2 fully counterclockwise.
- Tune the radio to where you want the low end of the FM band to be (probably around 550kHz).
- The voltage should be quite low, 10-20mV or so, Rotate RV2 CW until the voltage just starts to rise, no more than 80mV.
- Tune the radio to where you want the high end of the FM band to be (probably around 1600kHz).
- Adjust RV10 until the voltage 1.0V.
- You're done. As you tune the radio across the band, you should hear all your local FM stations!