

Gord's Superregen FM receiver runs from 24V

- I've never made a superregenerative receiver. The OVRC meeting about 1-tube radios inspired me to try.
- I decided to see if I could do it with low plate voltage. Just for fun.
- Superregen part is based on several Popular Electronics articles from the 60's.
- The results are surprisingly good, though since it uses "slope detection" distortion is a bit high and tuning is fussy. However, in my kitchen, it picks up all local stations without an antenna.
- Surprisingly, drift does not seem to be an issue.
- It is fairly loud, the 26A7GT can deliver about a half watt of audio.



Superregen


1st Audio

2nd Audio

3rd Audio

Phase Splitter

P-P Output

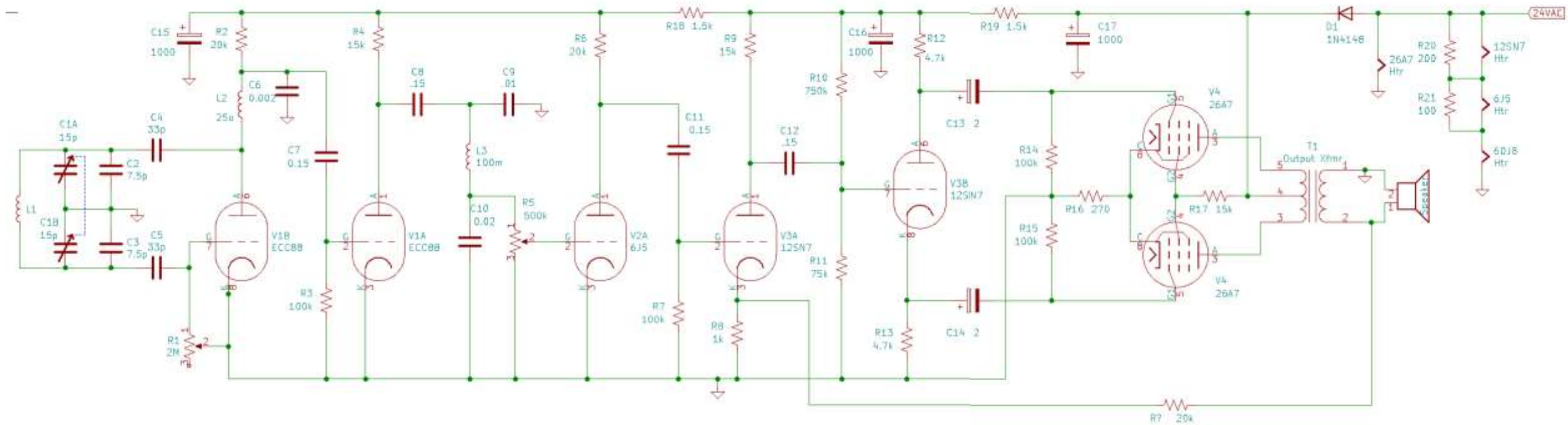


Superregenerative FM Receiver, Operates from 24VAC

Design Notes

- The magic all happens in and around the first triode.
- Keep leads short and direct. Use a ground plane.
- R1 sets the quenching frequency. Adjust for best performance.
- Adjust L1 until you get coverage of the FM band.
- I wanted a 6GM8 tube that is designed to work with 12V on the plate, but couldn't find one. A 6DJ8 is pretty close.

2.75 turns of #14 house wire
about 1 inch internal diameter

Keep these leads short and direct

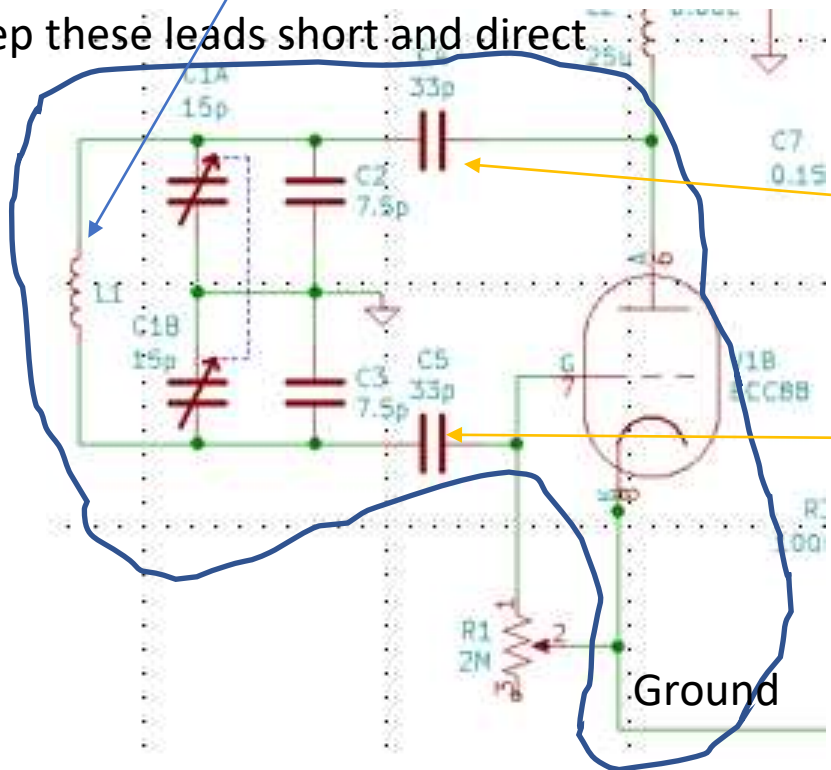

Note brass ground plane



I used a ceramic socket, but that's probably not necessary

Design Notes

- Yes, that is a 100mH choke! I found too much of the quench signal getting all the way to the output and this choke killed it completely.
- I probably have one audio stage too many. There is plenty of gain.
- I used a 26A7GT for the output, a tube designed to produce acceptable audio power from a 26V supply. I used a random universal output transformer, played with the output taps for best performance.
- Feedback cleaned up some distortion, but lowered gain. You'll need to experiment with the phase of the output transformer to ensure negative feedback. Positive feedback=oscillation!

Design Notes


- Note that the 6DJ8 takes an odd filament current: 360mA, so the 100 ohm and 200 ohm resistors around the other filaments ensure the voltage is shared properly.
- You will want to shield the filament wire around V1 to prevent it from inducing hum.
- Please do not analyze this circuit or assume it has been optimized. It was thrown together on the bench with available parts!

For Reference

Triode currents at low plate voltage

			Current at	plate volta
E80CC	6085		3.5	50
ECC80	none!			
ECC81	12AT7		2	50
ECC82	12AU7		5	50
ECC83	12AX7			
ECC84	6CW7			
ECC85	6AQ8			
ECC86	6GM8		4	10
ECC87	ECC40	"Military"		
ECC88	6DJ8		15	50
ECC89	6FC7			
ECC91	6J6		5	50
ECC180	6BQ7		7.5	50
ECC186	12AU7			
ECC189	6ES8			
DCC90	3A5		2.5	50
	6AF4		22	50
	9002		4	50
	8056	nuvistor	6	10
8393	7586		18	50
	957	filament ac	1.5	50

Pocket FM Receiver

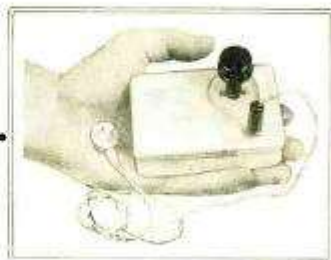

By HERB COHEN*

HERE'S a miniature FM receiver that requires no external antenna, uses only one miniature tube and has good fidelity. The entire FM broadcast band is covered with enough selectivity to separate weak from strong signals even in metropolitan areas.

And it's possible to complete this "under \$10.00" project in just one evening. Component placement is not critical even though the radio is constructed within a plastic case that is no larger than a cigarette pack.

Construction. The subminiature 1AG4 tube socket should be pre-wired before installation. Follow detail view, soldering plate and screen lugs together and then connecting 2½" lengths of hookup wire as shown. Connect C2, C3 and R1 directly to the grid lug. The tube socket can be glued directly to the case with a drop of Duco cement.

Antenna coil L1 is made by winding four turns of #14 gauge solid wire around a form ¾" in diameter. The turns should be spaced as close together as possible without actually touching each other. Remove L1 from the form and solder its two ends directly across tuning capacitor C1. All leads should be as short as possible.

Quench coil L2 is a four-section 2.5-mh. choke. Tap into L2 between the first and second section as shown. Then carefully scrape the connecting wire clean and solder a thin flexible 3" lead to the tap.

All components can now be screwed or glued into place. In order to eliminate hand capacitance effect, an insulated shaft extension is used with C1. A dynamic ear-

phone of 2000-3000 ohms impedance should be plugged into J1.


Trouble-Shooting. Before turning the unit on, check for shorts in the wiring. Turn C1 to full mesh and S1 to the "on" position. If the unit is functioning, a loud hiss will be heard. Tune C1 across the band until the hiss subsides and a station appears. A large dead area may appear at the high end of the FM band. If this happens, shorten the leads in the tuning circuit.

If a hiss is not heard, touch C1 with an insulated screwdriver. A click should be heard indicating that the ultra-audio section is oscillating but the quench circuitry is not functioning. Check all components, particularly the tap on L2, for a short, break or wiring error. Check battery voltage—if B2 drops below 1.3 volts, oscillation will be difficult to obtain.

One method of calibrating your set to cover the entire FM band is to place the pocket receiver near a commercial FM set. Tune the commercial FM receiver to 88 mc. Then tune C1 until a rushing noise is heard. Mark this spot on the pocket receiver's case. Repeat this procedure for the upper end of the FM band at 108 mc. If the high


(Continued on page 112)

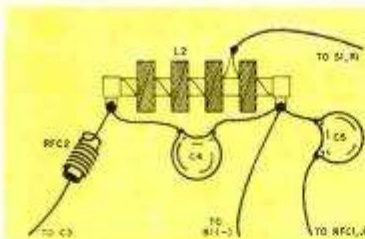*General Transistor Corp., Applications Engineering Dept.
POPULAR ELECTRONICS




Wiring details of quench oscillator coil L2. Note added coil tap.

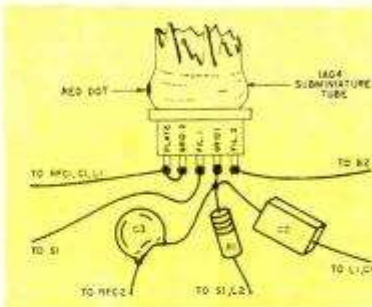Detail view of wiring of subminiature tube socket. Red dot on tube is guide for proper installation.



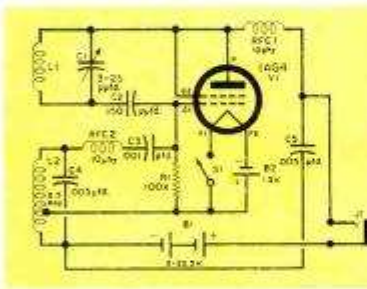
Sensitive superregen circuit pulls in FM band—without an antenna



PARTS LIST

- B1—2.22.5 volt battery (Burgess Y15)
- B2—1.5-volt penlight cell
- C1—0.001-μfd. variable capacitor (Hammarlund APC-35)
- C2—150-μfd. mica capacitor
- C3—0.001-μfd. disc ceramic capacitor
- C4, C5—0.005-μfd. disc ceramic capacitor
- J1—Miniature open-circuit phone jack
- L1—Four turns of #14 solid wire (see text)
- L2—2.5-mh. choke (Miller 4537)
- R1—100,000-ohm, ½-watt resistor
- RFC1, RFC2—10-μh. choke (Miller 4512)
- S1—S.p.s.t. slide switch
- V1—1AG4 electron tube
- 1—Plastic shaft extension
- 2—Battery holders (Acme 3 and Acme 45)
- 3—Subminiature tube socket

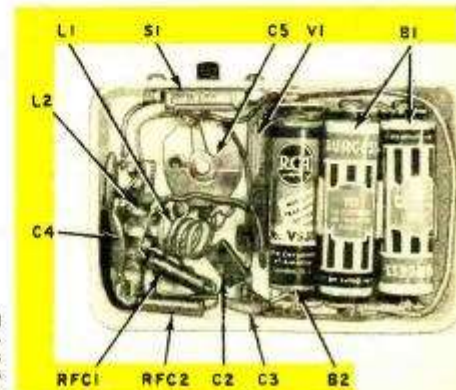Antenna coil L1 is the only one requiring special winding. All others are commercially available. For longer battery life, a mercury cell can be used as B2 instead of standard penlight cell.



Parts placement shown should be followed carefully for best results. Consult the two detail views above for exact positions. All leads should be as short as possible.

FM in Your Pocket

(Continued from page 36)

end of the band does not come through, spread the turns of the tuning coil L1 slightly. Compress to obtain the low end of the band.

In order to increase sensitivity in very weak signal areas, place the receiver near any metal surface. This method of loose coupling utilizes the metal object as an antenna.


HOW IT WORKS

Through the use of a superregenerative type detector, gain comparable to a full superheterodyne receiver has been obtained. The circuit utilizes two separate oscillators. The first, an r.f. ultra-audio (200 mc.) oscillator, is tuned by L1 and C1 in the tuning r.f. circuit. The inductively coupled capacitor of V1 is used to provide the feedback to sustain the oscillation. A quench oscillator of the Hartley type, whose tank circuit is L2 and C4, supplies the grid current at V1 on and off at a 30-40 cps. Its only purpose is to interrupt the high-frequency oscillation.


An r.f. signal appearing in the tank circuit triggers the ultra-audio oscillation on before its natural period and keeps it on slightly after the quench frequency would naturally kill it. The "extra" period of oscillation by the ultra-audio section results in a large phase current change. This current appears as the audio signal to the earphone. Since the incoming r.f. signal is used only as a trigger to fire the high-frequency oscillation, the overall gain of the circuit is not dependent either on the strength of the incoming signal or the gain of the tube.

ways say you saw it in—POPULAR ELECTRONICS


Superregenerative FM Receiver

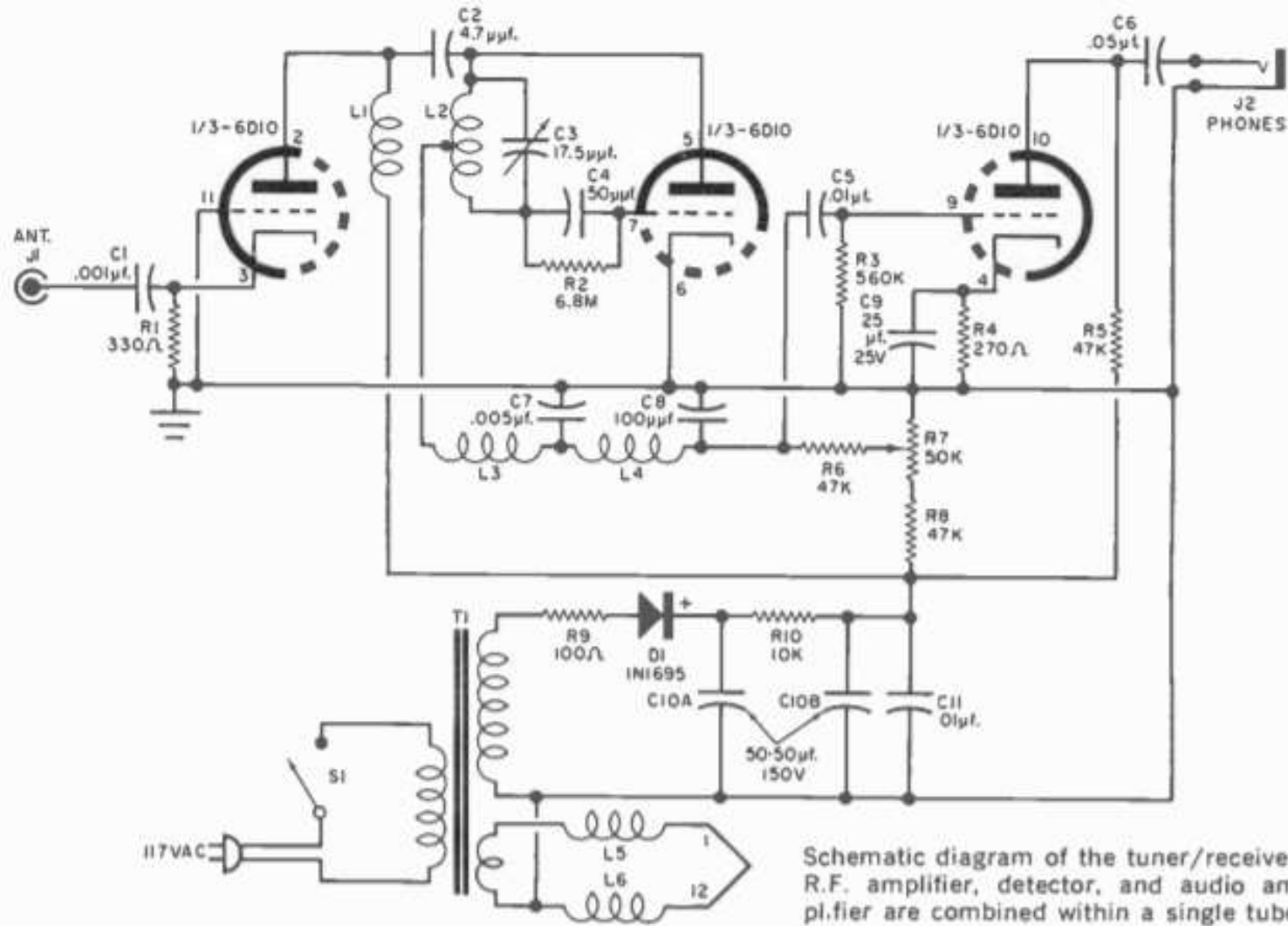

August 1961
Popular Electronics

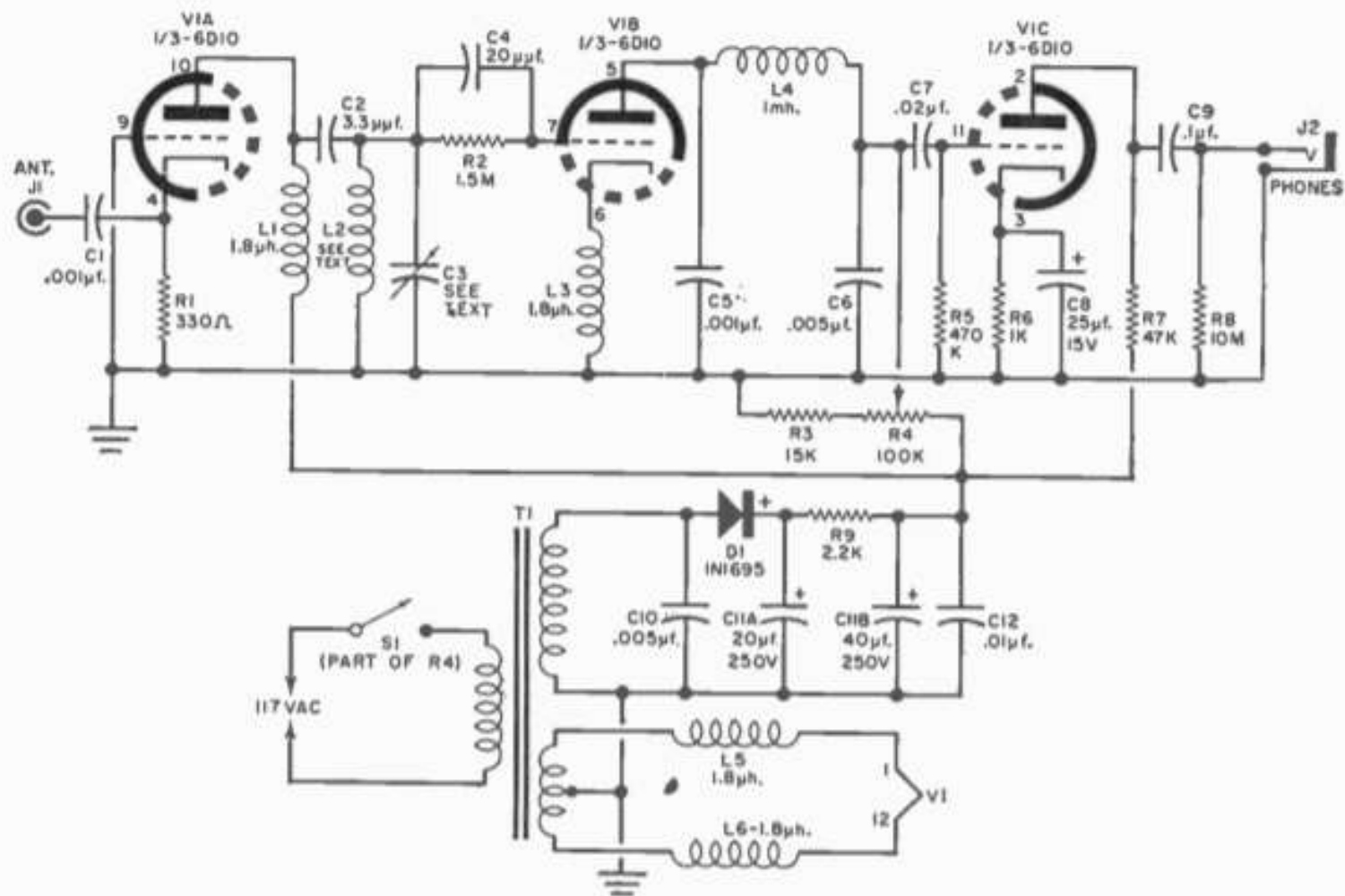

Sept 1961 PE

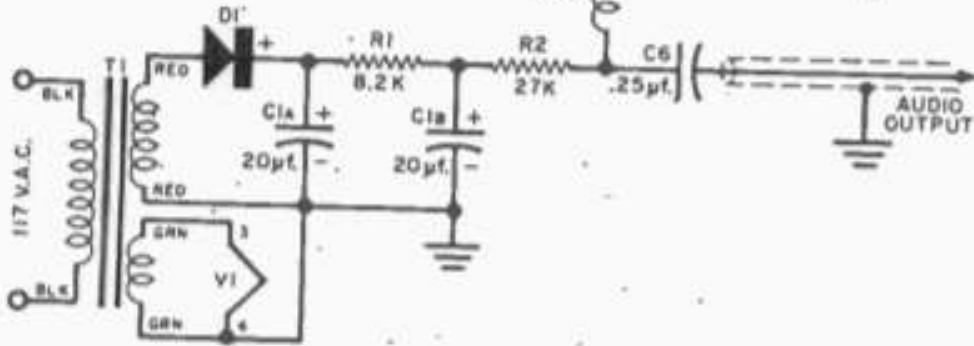

Aug 1960
Popular
Electronics